

45. Starting with zero current at $t = 0$ (the moment the switch is closed) the current in the circuit increases according to

$$i = \frac{\mathcal{E}}{R} \left(1 - e^{-t/\tau_L} \right) ,$$

where $\tau_L = L/R$ is the inductive time constant and \mathcal{E} is the battery emf. To calculate the time at which $i = 0.9990\mathcal{E}/R$, we solve for t :

$$0.9990 \frac{\mathcal{E}}{R} = \frac{\mathcal{E}}{R} \left(1 - e^{-t/\tau_L} \right) \implies \ln(0.0010) = -(t/\tau) \implies t = 6.91\tau_L .$$