

27. The assumption stated at the end of the problem is equivalent to setting  $\phi = 0$  in Eq. 33-25. Since the maximum energy in the capacitor (each cycle) is given by  $q_{\max}^2/2C$ , where  $q_{\max}$  is the maximum charge (during a given cycle), then we seek the time for which

$$\frac{q_{\max}^2}{2C} = \frac{1}{2} \frac{Q^2}{2C} \implies q_{\max} = \frac{Q}{\sqrt{2}} .$$

Now  $q_{\max}$  (referred to as the *exponentially decaying amplitude* in §33-5) is related to  $Q$  (and the other parameters of the circuit) by

$$q_{\max} = Qe^{-Rt/2L} \implies \ln\left(\frac{q_{\max}}{Q}\right) = -\frac{Rt}{2L} .$$

Setting  $q_{\max} = Q/\sqrt{2}$ , we solve for  $t$ :

$$t = -\frac{2L}{R} \ln\left(\frac{q_{\max}}{Q}\right) = -\frac{2L}{R} \ln\left(\frac{1}{\sqrt{2}}\right) = \frac{L}{R} \ln 2 .$$

The identities  $\ln(1/\sqrt{2}) = -\ln \sqrt{2} = -\frac{1}{2} \ln 2$  were used to obtain the final form of the result.