

32. (a) and (b) Regardless of the frequency of the generator, the current through the resistor is

$$I = \frac{\mathcal{E}_m}{R} = \frac{30.0 \text{ V}}{50 \Omega} = 0.60 \text{ A} .$$