

4. (a) Since $\mathcal{E}_1 > \mathcal{E}_2$ the current flows counterclockwise.
(b) Battery 1, since the current flows through it from its negative terminal to the positive one.
(c) Point B , since the current flows from B to A .