

82. The part of  $R_0$  connected in parallel with  $R$  is given by  $R_1 = R_0 x/L$ , where  $L = 10$  cm. The voltage difference across  $R$  is then  $V_R = \mathcal{E}R'/R_{\text{eq}}$ , where  $R' = RR_1/(R + R_1)$  and  $R_{\text{eq}} = R_0(1 - x/L) + R'$ . Thus

$$P_R = \frac{V_R^2}{R} = \frac{1}{R} \left( \frac{\mathcal{E}RR_1/(R + R_1)}{R_0(1 - x/L) + RR_1/(R + R_1)} \right)^2 .$$

Algebraic manipulation then leads to

$$P_R = \frac{100R(\mathcal{E}x/R_0)^2}{(100R/R_0 + 10x - x^2)^2}$$

where  $x$  is measured in cm.