

90. (a) We observe that  $\omega = 7540 \text{ rad/s}$ , and, consequently,  $X_L = 377 \Omega$  and  $X_C = 15.3 \Omega$ . Therefore, Eq. 33-64 leads to

$$I_{\text{rms}} = \frac{112 \text{ V}}{\sqrt{(35 \Omega)^2 + (377 \Omega - 15 \Omega)^2}} = 0.308 \text{ A} .$$

- (b) (c) (d) (e) (f) and (g) For the individual elements, we have:

$$V_{R,\text{rms}} = I_{\text{rms}} R = 10.8 \text{ V}$$

$$V_{C,\text{rms}} = I_{\text{rms}} X_C = 4.73 \text{ V}$$

$$V_{L,\text{rms}} = I_{\text{rms}} X_L = 116 \text{ V}$$

The capacitor and inductor are not dissipative elements; the only power dissipated (by definition) is in the resistor. If a coil, perhaps referred to as an inductor in building a circuit, is found to have an internal resistance, then the coil (for purposes of analysis) is taken to be an inductor plus a resistor. The power dissipated in the resistive element is  $P_{\text{avg}} = (0.308 \text{ A})^2(35 \Omega) = 3.33 \text{ W}$ .