

34. (a) The circuit consists of one generator across one inductor; therefore, $\mathcal{E}_m = V_L$. The current amplitude is

$$I = \frac{\mathcal{E}_m}{X_L} = \frac{\mathcal{E}_m}{\omega_d L} = \frac{25.0 \text{ V}}{(377 \text{ rad/s})(12.7 \text{ H})} = 5.22 \times 10^{-3} \text{ A} .$$

- (b) When the current is at a maximum, its derivative is zero. Thus, Eq. 31-37 gives $\mathcal{E}_L = 0$ at that instant. Stated another way, since $\mathcal{E}(t)$ and $i(t)$ have a 90° phase difference, then $\mathcal{E}(t)$ must be zero when $i(t) = I$. The fact that $\phi = 90^\circ = \pi/2$ rad is used in part (c).
- (c) Consider Eq. 32-28 with $\mathcal{E} = -\frac{1}{2}\mathcal{E}_m$. In order to satisfy this equation, we require $\sin(\omega_d t) = -1/2$. Now we note that the problem states that \mathcal{E} is increasing *in magnitude*, which (since it is already negative) means that it is becoming more negative. Thus, differentiating Eq. 32-28 with respect to time (and demanding the result be negative) we must also require $\cos(\omega_d t) < 0$. These conditions imply that ωt must equal $(2n\pi - 5\pi/6)$ [$n = \text{integer}$]. Consequently, Eq. 33-29 yields (for all values of n)

$$i = I \sin\left(2n\pi - \frac{5\pi}{6} - \frac{\pi}{2}\right) = (5.22 \times 10^{-3} \text{ A}) \left(\frac{\sqrt{3}}{2}\right) = 4.51 \times 10^{-3} \text{ A} .$$