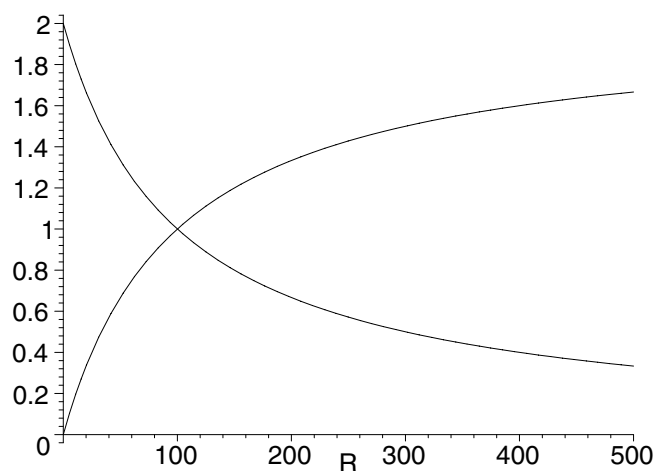


8. (a) Below, we graph Eq. 28-4 (scaled by a factor of 100) for  $\mathcal{E} = 2.0\text{ V}$  and  $r = 100\ \Omega$  over the range  $0 \leq R \leq 500\ \Omega$ . We multiplied the SI output of Eq. 28-4 by 100 so that this graph would not be vanishingly small with the other graph (see part (b)) when they are plotted together.
- (b) In the same graph, we show  $V_R = iR$  over the same range. The graph of current  $i$  is the one that starts at 2 (which corresponds to 0.02 A in SI units) and the graph of voltage  $V_R$  is the one that starts at 0 (when  $R = 0$ ). The value of  $V_R$  are in SI units (not scaled by any factor).



- (c) In our final graph, we show the dependence of power  $P = iV_R$  (dissipated in resistor  $R$ ) as a function of  $R$ . The units of the vertical axis are Watts. We note that it is maximum when  $R = r$ .

