

87. (a) We observe that $\omega = 6597 \text{ rad/s}$, and, consequently, $X_L = 594 \, \Omega$ and $X_C = 303 \, \Omega$. Since $X_L > X_C$, the phase angle is positive: $\phi = +60^\circ$.

- (b) From Eq. 33-65, we obtain

$$R = \frac{X_L - X_C}{\tan \phi} = 168 \, \Omega \quad .$$

- (c) Since we are already on the “high side” of resonance, increasing f will only decrease the current further, but *decreasing* f brings us closer to resonance and, consequently, large values of I .
- (d) Increasing L increases X_L , but we already have $X_L > X_C$. Thus, if we wish to move closer to resonance (where X_L must equal X_C), we need to *decrease* the value of L .
- (e) To change the present condition of $X_C < X_L$ to something closer to $X_C = X_L$ (resonance, large current), we can increase X_C . Since X_C depends inversely on C , this means *decreasing* C .