

57. In the first case the two capacitors are effectively connected in series, so the output potential difference is $V_{\text{out}} = CV_{\text{in}}/2C = V_{\text{in}}/2 = 50.0 \text{ V}$. In the second case the lower diode acts as a wire so $V_{\text{out}} = 0$.