

15. (a) Since the frequency of oscillation  $f$  is related to the inductance  $L$  and capacitance  $C$  by  $f = 1/2\pi\sqrt{LC}$ , the smaller value of  $C$  gives the larger value of  $f$ . Consequently,  $f_{\max} = 1/2\pi\sqrt{LC_{\min}}$ ,  $f_{\min} = 1/2\pi\sqrt{LC_{\max}}$ , and

$$\frac{f_{\max}}{f_{\min}} = \frac{\sqrt{C_{\max}}}{\sqrt{C_{\min}}} = \frac{\sqrt{365 \text{ pF}}}{\sqrt{10 \text{ pF}}} = 6.0 .$$

- (b) An additional capacitance  $C$  is chosen so the ratio of the frequencies is

$$r = \frac{1.60 \text{ MHz}}{0.54 \text{ MHz}} = 2.96 .$$

Since the additional capacitor is in parallel with the tuning capacitor, its capacitance adds to that of the tuning capacitor. If  $C$  is in picofarads, then

$$\frac{\sqrt{C + 365 \text{ pF}}}{\sqrt{C + 10 \text{ pF}}} = 2.96 .$$

The solution for  $C$  is

$$C = \frac{(365 \text{ pF}) - (2.96)^2(10 \text{ pF})}{(2.96)^2 - 1} = 36 \text{ pF} .$$

We solve  $f = 1/2\pi\sqrt{LC}$  for  $L$ . For the minimum frequency  $C = 365 \text{ pF} + 36 \text{ pF} = 401 \text{ pF}$  and  $f = 0.54 \text{ MHz}$ . Thus

$$L = \frac{1}{(2\pi)^2 C f^2} = \frac{1}{(2\pi)^2 (401 \times 10^{-12} \text{ F})(0.54 \times 10^6 \text{ Hz})^2} = 2.2 \times 10^{-4} \text{ H} .$$