

84. (a) Using  $X_C = 1/\omega C$  and  $V_C = I_C X_C$ , we find

$$\omega = \frac{I_C}{CV_C} = 5.77 \times 10^5 \text{ rad/s} .$$

This value is used in the subsequent parts. The period is  $T = 2\pi/\omega = 1.09 \times 10^{-5} \text{ s}$ .

- (b) Adapting Eq. 26-22 to the notation of this chapter,

$$U_{E,\max} = \frac{1}{2}CV_C^2 = 4.5 \times 10^{-9} \text{ J} .$$

- (c) The discussion in §33-4 shows that  $U_{E,\max} = U_{B,\max}$ .

- (d) We return to Eq. 31-37 (though other, equivalent, approaches could be explored):

$$\frac{di}{dt} = \frac{-\mathcal{E}_L}{L}$$

By the loop rule,  $\mathcal{E}_L$  is at its most negative value when the capacitor voltage is at its most positive ( $V_C$ ). Using this plus the frequency relationship between  $L$  and  $C$  (Eq. 33-4) leads to

$$\left| \frac{di}{dt} \right|_{\max} = \omega^2 CV_C = 998 \text{ A/s} .$$

- (e) Differentiating Eq. 31-51, we have

$$\frac{dU_B}{dt} = Li \frac{di}{dt} .$$

As in the previous part, we use  $L = 1/\omega^2 C$ . We also use a simple sinusoidal form for the current,  $i = I \sin \omega t$ :

$$\frac{dU_B}{dt} = \frac{1}{\omega^2 C} I^2 \omega \sin \omega t \cos \omega t$$

where this  $I$  is equivalent to the  $I_C$  used in part (a). Using a well-known trig identity, we obtain

$$\left( \frac{dU_B}{dt} \right)_{\max} = \frac{I^2}{2\omega^2 C} (\sin 2\omega t)_{\max} = \frac{I^2}{2\omega^2 C}$$

which yields a (maximum) time rate of change (for  $U_B$ ) equal to  $2.60 \times 10^{-3} \text{ J/s}$ .