

57. (a) The power factor is $\cos \phi$, where ϕ is the phase constant defined by the expression $i = I \sin(\omega t - \phi)$. Thus, $\phi = -42.0^\circ$ and $\cos \phi = \cos(-42.0^\circ) = 0.743$.
- (b) Since $\phi < 0$, $\omega t - \phi > \omega t$. The current leads the emf.
- (c) The phase constant is related to the reactance difference by $\tan \phi = (X_L - X_C)/R$. We have $\tan \phi = \tan(-42.0^\circ) = -0.900$, a negative number. Therefore, $X_L - X_C$ is negative, which leads to $X_C > X_L$. The circuit in the box is predominantly capacitive.
- (d) If the circuit were in resonance X_L would be the same as X_C , $\tan \phi$ would be zero, and ϕ would be zero. Since ϕ is not zero, we conclude the circuit is not in resonance.
- (e) Since $\tan \phi$ is negative and finite, neither the capacitive reactance nor the resistance are zero. This means the box must contain a capacitor and a resistor. The inductive reactance may be zero, so there need not be an inductor. If there is an inductor its reactance must be less than that of the capacitor at the operating frequency.
- (f) The average power is

$$P_{\text{avg}} = \frac{1}{2} \mathcal{E}_m I \cos \phi = \frac{1}{2} (75.0 \text{ V})(1.20 \text{ A})(0.743) = 33.4 \text{ W} .$$

- (g) The answers above depend on the frequency only through the phase constant ϕ , which is given. If values were given for R , L and C then the value of the frequency would also be needed to compute the power factor.