

42. (a) We note that we obtain the maximum value in Eq. 33-28 when we set

$$t = \frac{\pi}{2\omega_d} = \frac{1}{4f} = \frac{1}{4(60)} = 0.00417 \text{ s}$$

or 4.17 ms. The result is $\mathcal{E}_m \sin(\pi/2) = \mathcal{E}_m \sin(90^\circ) = 36.0 \text{ V}$. We note, for reference in the subsequent parts, that at $t = 4.17 \text{ ms}$, the current is

$$i = I \sin(\omega_d t - \phi) = I \sin(90^\circ - (-29.4^\circ)) = (0.196 \text{ A}) \cos(29.4^\circ) = 0.171 \text{ A}$$

using Eq. 33-29 and the results of the Sample Problem.

- (b) At $t = 4.17 \text{ ms}$, Ohm's law directly gives

$$v_R = iR = (I \cos(29.4^\circ)) R(0.171 \text{ A})(160 \Omega) = 27.3 \text{ V} .$$

- (c) The capacitor voltage phasor is 90° less than that of the current. Thus, at $t = 4.17 \text{ ms}$, we obtain

$$v_C = I \sin(90^\circ - (-29.4^\circ) - 90^\circ) X_C = I X_C \sin(29.4^\circ) = (0.196 \text{ A})(177 \Omega) \sin(29.4^\circ) = 17.0 \text{ V} .$$

- (d) The inductor voltage phasor is 90° more than that of the current. Therefore, at $t = 4.17 \text{ ms}$, we find

$$v_L = I \sin(90^\circ - (-29.4^\circ) + 90^\circ) X_L = -I X_L \sin(29.4^\circ) = -(0.196 \text{ A})(86.7 \Omega) \sin(29.4^\circ) = -8.3 \text{ V} .$$

- (e) Our results for parts (b), (c) and (d) add to give 36.0 V , the same as the answer for part (a).