

76. For  $t < 0$ , no current goes through  $L_2$ , so  $i_2 = 0$  and  $i_1 = \mathcal{E}/R$ . As the switch is opened there will be a very brief sparking across the gap.  $i_1$  drops while  $i_2$  increases, both very quickly. The loop rule can be written as

$$\mathcal{E} - i_1 R - L_1 \frac{di_1}{dt} - i_2 R - L_2 \frac{di_2}{dt} = 0 ,$$

where the initial value of  $i_1$  at  $t = 0$  is given by  $\mathcal{E}/R$  and that of  $i_2$  at  $t = 0$  is 0. We consider the situation shortly after  $t = 0$ . Since the sparking is very brief, we can reasonably assume that both  $i_1$  and  $i_2$  get equalized quickly, before they can change appreciably from their respective initial values. Here, the loop rule requires that  $L_1(di_1/dt)$ , which is large and negative, must roughly cancel  $L_2(di_2/dt)$ , which is large and positive:

$$L_1 \frac{di_1}{dt} \approx -L_2 \frac{di_2}{dt} .$$

Let the common value reached by  $i_1$  and  $i_2$  be  $i$ , then

$$\frac{di_1}{dt} \approx \frac{\Delta i_1}{\Delta t} = \frac{i - \mathcal{E}/R}{\Delta t}$$

and

$$\frac{di_2}{dt} \approx \frac{\Delta i_2}{\Delta t} = \frac{i - 0}{\Delta t} .$$

The equations above yield

$$L_1 \left( i - \frac{\mathcal{E}}{R} \right) = -L_2(i - 0) \implies i = \frac{\mathcal{E}L_1}{L_2R_1 + L_1R_2} = \frac{L_1}{L_1 + L_2} \frac{\mathcal{E}}{R} .$$