

1. (a) The cost is $(100 \text{ W} \cdot 8.0 \text{ h} / 2.0 \text{ W} \cdot \text{h}) (\$0.80) = \$3.2 \times 10^2$.

(b) The cost is $(100 \text{ W} \cdot 8.0 \text{ h} / 10^3 \text{ W} \cdot \text{h}) (\$0.06) = \$0.048 = 4.8 \text{ cents}$.

2. The chemical energy of the battery is reduced by $\Delta E = q\mathcal{E}$, where q is the charge that passes through in time $\Delta t = 6.0$ min, and \mathcal{E} is the emf of the battery. If i is the current, then $q = i \Delta t$ and

$$\Delta E = i\mathcal{E} \Delta t = (5.0 \text{ A})(6.0 \text{ V}) (6.0 \text{ min}) (60 \text{ s/min}) = 1.1 \times 10^4 \text{ J}.$$

We note the conversion of time from minutes to seconds.

3. If P is the rate at which the battery delivers energy and Δt is the time, then $\Delta E = P \Delta t$ is the energy delivered in time Δt . If q is the charge that passes through the battery in time Δt and \mathcal{E} is the emf of the battery, then $\Delta E = q\mathcal{E}$. Equating the two expressions for ΔE and solving for Δt , we obtain

$$\Delta t = \frac{q\mathcal{E}}{P} = \frac{(120 \text{ A} \cdot \text{h})(12.0 \text{ V})}{100 \text{ W}} = 14.4 \text{ h}.$$

4. (a) The energy transferred is

$$U = Pt = \frac{\mathcal{E}^2 t}{r + R} = \frac{(2.0 \text{ V})^2 (2.0 \text{ min})(60 \text{ s/min})}{1.0 \Omega + 5.0 \Omega} = 80 \text{ J}.$$

(b) The amount of thermal energy generated is

$$U' = i^2 R t = \left(\frac{\mathcal{E}}{r + R} \right)^2 R t = \left(\frac{2.0 \text{ V}}{1.0 \Omega + 5.0 \Omega} \right)^2 (5.0 \Omega) (2.0 \text{ min})(60 \text{ s/min}) = 67 \text{ J}.$$

(c) The difference between U and U' , which is equal to 13 J, is the thermal energy that is generated in the battery due to its internal resistance.

5. (a) Let i be the current in the circuit and take it to be positive if it is to the left in R_1 . We use Kirchhoff's loop rule: $\mathcal{E}_1 - iR_2 - iR_1 - \mathcal{E}_2 = 0$. We solve for i :

$$i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2} = \frac{12 \text{ V} - 6.0 \text{ V}}{4.0 \Omega + 8.0 \Omega} = 0.50 \text{ A}.$$

A positive value is obtained, so the current is counterclockwise around the circuit.

If i is the current in a resistor R , then the power dissipated by that resistor is given by $P = i^2 R$.

(b) For R_1 , $P_1 = (0.50 \text{ A})^2 (4.0 \Omega) = 1.0 \text{ W}$,

(c) and for R_2 , $P_2 = (0.50 \text{ A})^2 (8.0 \Omega) = 2.0 \text{ W}$.

If i is the current in a battery with emf \mathcal{E} , then the battery supplies energy at the rate $P = i\mathcal{E}$ provided the current and emf are in the same direction. The battery absorbs energy at the rate $P = i\mathcal{E}$ if the current and emf are in opposite directions.

(d) For \mathcal{E}_1 , $P_1 = (0.50 \text{ A})(12 \text{ V}) = 6.0 \text{ W}$

(e) and for \mathcal{E}_2 , $P_2 = (0.50 \text{ A})(6.0 \text{ V}) = 3.0 \text{ W}$.

(f) In battery 1 the current is in the same direction as the emf. Therefore, this battery supplies energy to the circuit; the battery is discharging.

(g) The current in battery 2 is opposite the direction of the emf, so this battery absorbs energy from the circuit. It is charging.

6. The current in the circuit is

$$i = (150 \text{ V} - 50 \text{ V}) / (3.0 \, \Omega + 2.0 \, \Omega) = 20 \text{ A}.$$

So from $V_Q + 150 \text{ V} - (2.0 \, \Omega)i = V_P$, we get $V_Q = 100 \text{ V} + (2.0 \, \Omega)(20 \text{ A}) - 150 \text{ V} = -10 \text{ V}$.

7. (a) The potential difference is $V = \mathcal{E} + ir = 12 \text{ V} + (0.040 \text{ } \Omega)(50 \text{ A}) = 14 \text{ V}$.

(b) $P = i^2 r = (50 \text{ A})^2 (0.040 \text{ } \Omega) = 1.0 \times 10^2 \text{ W}$.

(c) $P' = iV = (50 \text{ A})(12 \text{ V}) = 6.0 \times 10^2 \text{ W}$.

(d) In this case $V = \mathcal{E} - ir = 12 \text{ V} - (0.040 \text{ } \Omega)(50 \text{ A}) = 10 \text{ V}$.

(e) $P_r = i^2 r = 1.0 \times 10^2 \text{ W}$.

8. (a) We solve $i = (\mathcal{E}_2 - \mathcal{E}_1)/(r_1 + r_2 + R)$ for R :

$$R = \frac{\mathcal{E}_2 - \mathcal{E}_1}{i} - r_1 - r_2 = \frac{3.0 \text{ V} - 2.0 \text{ V}}{1.0 \times 10^{-3} \text{ A}} - 3.0 \Omega - 3.0 \Omega = 9.9 \times 10^2 \Omega.$$

(b) $P = i^2 R = (1.0 \times 10^{-3} \text{ A})^2 (9.9 \times 10^2 \Omega) = 9.9 \times 10^{-4} \text{ W}.$

9. (a) If i is the current and ΔV is the potential difference, then the power absorbed is given by $P = i \Delta V$. Thus,

$$\Delta V = \frac{P}{i} = \frac{50 \text{ W}}{1.0 \text{ A}} = 50 \text{ V}.$$

Since the energy of the charge decreases, point A is at a higher potential than point B; that is, $V_A - V_B = 50 \text{ V}$.

(b) The end-to-end potential difference is given by $V_A - V_B = +iR + \mathcal{E}$, where \mathcal{E} is the emf of element C and is taken to be positive if it is to the left in the diagram. Thus,

$$\mathcal{E} = V_A - V_B - iR = 50 \text{ V} - (1.0 \text{ A})(2.0 \Omega) = 48 \text{ V}.$$

(c) A positive value was obtained for \mathcal{E} , so it is toward the left. The negative terminal is at B.

10. (a) For each wire, $R_{\text{wire}} = \rho L/A$ where $A = \pi r^2$. Consequently, we have

$$R_{\text{wire}} = (1.69 \times 10^{-8})(0.200)/\pi(0.00100)^2 = 0.0011 \, \Omega.$$

The total resistive load on the battery is therefore $2R_{\text{wire}} + 6.00 \, \Omega$. Dividing this into the battery emf gives the current $i = 1.9993 \, \text{A}$. The voltage across the $6.00 \, \Omega$ resistor is therefore $(1.9993 \, \text{A})(6.00 \, \Omega) = 11.996 \, \text{V} \approx 12 \, \text{V}$.

(b) Similarly, we find the voltage-drop across each wire to be $2.15 \, \text{mV}$.

(c) $P = i^2 R = (1.9993 \, \text{A})(6 \, \Omega)^2 = 23.98 \, \text{W} \approx 24.0 \, \text{W}$.

(d) Similarly, we find the power dissipated in each wire to be $4.30 \, \text{mW}$.

11. Let the emf be \mathcal{V} . Then $\mathcal{V} = iR = i'(R + R')$, where $i = 5.0$ A, $i' = 4.0$ A and $R' = 2.0\ \Omega$. We solve for R :

$$R = \frac{i'R'}{i - i'} = \frac{(4.0)(2.0)}{5.0 - 4.0} = 8.0\ \Omega.$$

12. (a) Here we denote the battery emf's as V_1 and V_2 . The loop rule gives

$$V_2 - ir_2 + V_1 - ir_1 - iR = 0 \quad \Rightarrow \quad i = \frac{V_2 + V_1}{r_1 + r_2 + R} .$$

The terminal voltage of battery 1 is V_{1T} and (see Fig. 27-4(a)) is easily seen to be equal to $V_1 - ir_1$; similarly for battery 2. Thus,

$$V_{1T} = V_1 - \frac{r_1(V_2 + V_1)}{r_1 + r_2 + R} \quad \text{and} \quad V_{2T} = V_2 - \frac{r_2(V_2 + V_1)}{r_1 + r_2 + R} .$$

The problem tells us that V_1 and V_2 each equal 1.20 V. From the graph in Fig. 27-30(b) we see that $V_{2T} = 0$ and $V_{1T} = 0.40$ V for $R = 0.10 \, \Omega$. This supplies us (in view of the above relations for terminal voltages) with simultaneous equations, which, when solved, lead to $r_1 = 0.20 \, \Omega$.

(b) The simultaneous solution also gives $r_2 = 0.30 \, \Omega$.

13. To be as general as possible, we refer to the individual emf's as \mathcal{E}_1 and \mathcal{E}_2 and wait until the latter steps to equate them ($\mathcal{E}_1 = \mathcal{E}_2 = \mathcal{E}$). The batteries are placed in series in such a way that their voltages add; that is, they do not “oppose” each other. The total resistance in the circuit is therefore $R_{\text{total}} = R + r_1 + r_2$ (where the problem tells us $r_1 > r_2$), and the “net emf” in the circuit is $\mathcal{E}_1 + \mathcal{E}_2$. Since battery 1 has the higher internal resistance, it is the one capable of having a zero terminal voltage, as the computation in part (a) shows.

(a) The current in the circuit is

$$i = \frac{\mathcal{E}_1 + \mathcal{E}_2}{r_1 + r_2 + R},$$

and the requirement of zero terminal voltage leads to

$$\mathcal{E}_1 = ir_1 \Rightarrow R = \frac{\mathcal{E}_2 r_1 - \mathcal{E}_1 r_2}{\mathcal{E}_1} = \frac{(12.0)(0.016) - (12.0)(0.012)}{12.0} = 0.004 \, \Omega$$

Note that $R = r_1 - r_2$ when we set $\mathcal{E}_1 = \mathcal{E}_2$.

(b) As mentioned above, this occurs in battery 1.

14. (a) Let the emf of the solar cell be \mathcal{E} and the output voltage be V . Thus,

$$V = \mathcal{E} - ir = \mathcal{E} - \left(\frac{V}{R}\right)r$$

for both cases. Numerically, we get

$$\begin{aligned} 0.10 \text{ V} &= \mathcal{E} - (0.10 \text{ V}/500 \Omega)r \\ 0.15 \text{ V} &= \mathcal{E} - (0.15 \text{ V}/1000 \Omega)r. \end{aligned}$$

We solve for \mathcal{E} and r .

(a) $r = 1.0 \times 10^3 \Omega$.

(b) $\mathcal{E} = 0.30 \text{ V}$.

(c) The efficiency is

$$\frac{V^2 / R}{P_{\text{received}}} = \frac{0.15 \text{ V}}{(1000 \Omega) (5.0 \text{ cm}^2) (2.0 \times 10^{-3} \text{ W/cm}^2)} = 2.3 \times 10^{-3} = 0.23\%.$$

15. The potential difference across each resistor is $V = 25.0 \text{ V}$. Since the resistors are identical, the current in each one is $i = V/R = (25.0 \text{ V})/(18.0 \text{ } \Omega) = 1.39 \text{ A}$. The total current through the battery is then $i_{\text{total}} = 4(1.39 \text{ A}) = 5.56 \text{ A}$. One might alternatively use the idea of equivalent resistance; for four identical resistors in parallel the equivalent resistance is given by

$$\frac{1}{R_{\text{eq}}} = \sum \frac{1}{R} = \frac{4}{R}.$$

When a potential difference of 25.0 V is applied to the equivalent resistor, the current through it is the same as the total current through the four resistors in parallel. Thus

$$i_{\text{total}} = V/R_{\text{eq}} = 4V/R = 4(25.0 \text{ V})/(18.0 \text{ } \Omega) = 5.56 \text{ A}.$$

16. Let the resistances of the two resistors be R_1 and R_2 , with $R_1 < R_2$. From the statements of the problem, we have

$$R_1 R_2 / (R_1 + R_2) = 3.0 \, \Omega \text{ and } R_1 + R_2 = 16 \, \Omega.$$

So R_1 and R_2 must be $4.0 \, \Omega$ and $12 \, \Omega$, respectively.

(a) The smaller resistance is $R_1 = 4.0 \, \Omega$.

(b) The larger resistance is $R_2 = 12 \, \Omega$.

17. We note that two resistors in parallel, R_1 and R_2 , are equivalent to

$$R_{12} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}.$$

This situation (Figure 27-32) consists of a parallel pair which are then in series with a single $R_3 = 2.50 \, \Omega$ resistor. Thus, the situation has an equivalent resistance of

$$R_{\text{eq}} = R_3 + R_{12} = 2.50 \, \Omega + \frac{(4.00 \, \Omega)(4.00 \, \Omega)}{4.00 \, \Omega + 4.00 \, \Omega} = 4.50 \, \Omega.$$

18. (a) $R_{\text{eq}}(FH) = (10.0\ \Omega)(10.0\ \Omega)(5.00\ \Omega)/[(10.0\ \Omega)(10.0\ \Omega) + 2(10.0\ \Omega)(5.00\ \Omega)] = 2.50\ \Omega$.

(b) $R_{\text{eq}}(FG) = (5.00\ \Omega) R/(R + 5.00\ \Omega)$, where

$$R = 5.00\ \Omega + (5.00\ \Omega)(10.0\ \Omega)/(5.00\ \Omega + 10.0\ \Omega) = 8.33\ \Omega.$$

So $R_{\text{eq}}(FG) = (5.00\ \Omega)(8.33\ \Omega)/(5.00\ \Omega + 8.33\ \Omega) = 3.13\ \Omega$.

19. Let i_1 be the current in R_1 and take it to be positive if it is to the right. Let i_2 be the current in R_2 and take it to be positive if it is upward.

(a) When the loop rule is applied to the lower loop, the result is

$$\mathcal{E}_2 - i_1 R_1 = 0$$

The equation yields

$$i_1 = \frac{\mathcal{E}_2}{R_1} = \frac{5.0 \text{ V}}{100 \Omega} = 0.050 \text{ A}.$$

(b) When it is applied to the upper loop, the result is

$$\mathcal{E}_1 - \mathcal{E}_2 - \mathcal{E}_3 - i_2 R_2 = 0 .$$

The equation yields

$$i_2 = \frac{\mathcal{E}_1 - \mathcal{E}_2 - \mathcal{E}_3}{R_2} = \frac{6.0 \text{ V} - 5.0 \text{ V} - 4.0 \text{ V}}{50 \Omega} = -0.060 \text{ A} ,$$

or $|i_2| = 0.060 \text{ A}$. The negative sign indicates that the current in R_2 is actually downward.

(c) If V_b is the potential at point b , then the potential at point a is $V_a = V_b + \mathcal{E}_3 + \mathcal{E}_2$, so $V_a - V_b = \mathcal{E}_3 + \mathcal{E}_2 = 4.0 \text{ V} + 5.0 \text{ V} = 9.0 \text{ V}$.

20. The currents i_1 , i_2 and i_3 are obtained from Eqs. 27-18 through 27-20:

$$i_1 = \frac{\mathcal{E}_1(R_2 + R_3) - \mathcal{E}_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} = \frac{(4.0 \text{ V})(10 \Omega + 5.0 \Omega) - (1.0 \text{ V})(5.0 \Omega)}{(10 \Omega)(10 \Omega) + (10 \Omega)(5.0 \Omega) + (10 \Omega)(5.0 \Omega)} = 0.275 \text{ A} ,$$

$$i_2 = \frac{\mathcal{E}_1 R_3 - \mathcal{E}_2(R_1 + R_2)}{R_1 R_2 + R_2 R_3 + R_1 R_3} = \frac{(4.0 \text{ V})(5.0 \Omega) - (1.0 \text{ V})(10 \Omega + 5.0 \Omega)}{(10 \Omega)(10 \Omega) + (10 \Omega)(5.0 \Omega) + (10 \Omega)(5.0 \Omega)} = 0.025 \text{ A} ,$$

$$i_3 = i_2 - i_1 = 0.025 \text{ A} - 0.275 \text{ A} = -0.250 \text{ A} .$$

$V_d - V_c$ can now be calculated by taking various paths. Two examples: from $V_d - i_2 R_2 = V_c$ we get

$$V_d - V_c = i_2 R_2 = (0.0250 \text{ A}) (10 \Omega) = +0.25 \text{ V};$$

from $V_d + i_3 R_3 + \mathcal{E}_2 = V_c$ we get

$$V_d - V_c = i_3 R_3 - \mathcal{E}_2 = -(-0.250 \text{ A}) (5.0 \Omega) - 1.0 \text{ V} = +0.25 \text{ V}.$$

21. Let r be the resistance of each of the narrow wires. Since they are in parallel the resistance R of the composite is given by

$$\frac{1}{R} = \frac{9}{r},$$

or $R = r/9$. Now $r = 4\rho\ell / \pi d^2$ and $R = 4\rho\ell / \pi D^2$, where ρ is the resistivity of copper. $A = \pi d^2/4$ was used for the cross-sectional area of a single wire, and a similar expression was used for the cross-sectional area of the thick wire. Since the single thick wire is to have the same resistance as the composite,

$$\frac{4\rho\ell}{\pi D^2} = \frac{4\rho\ell}{9\pi d^2} \Rightarrow D = 3d.$$

22. Using the junction rule ($i_3 = i_1 + i_2$) we write two loop rule equations:

$$10.0 \text{ V} - i_1 R_1 - (i_1 + i_2) R_3 = 0$$

$$5.00 \text{ V} - i_2 R_2 - (i_1 + i_2) R_3 = 0.$$

(a) Solving, we find $i_2 = 0$, and

(b) $i_3 = i_1 + i_2 = 1.25 \text{ A}$ (downward, as was assumed in writing the equations as we did).

23. First, we note V_4 , that the voltage across R_4 is equal to the sum of the voltages across R_5 and R_6 :

$$V_4 = i_6(R_5 + R_6) = (1.40 \text{ A})(8.00 \, \Omega + 4.00 \, \Omega) = 16.8 \text{ V}.$$

The current through R_4 is then equal to $i_4 = V_4/R_4 = 16.8 \text{ V}/(16.0 \, \Omega) = 1.05 \text{ A}$.

By the junction rule, the current in R_2 is $i_2 = i_4 + i_6 = 1.05 \text{ A} + 1.40 \text{ A} = 2.45 \text{ A}$, so its voltage is $V_2 = (2.00 \, \Omega)(2.45 \text{ A}) = 4.90 \text{ V}$.

The loop rule tells us the voltage across R_3 is $V_3 = V_2 + V_4 = 21.7 \text{ V}$ (implying that the current through it is $i_3 = V_3/(2.00 \, \Omega) = 10.85 \text{ A}$).

The junction rule now gives the current in R_1 as $i_1 = i_2 + i_3 = 2.45 \text{ A} + 10.85 \text{ A} = 13.3 \text{ A}$, implying that the voltage across it is $V_1 = (13.3 \text{ A})(2.00 \, \Omega) = 26.6 \text{ V}$. Therefore, by the loop rule,

$$\mathcal{E} = V_1 + V_3 = 26.6 \text{ V} + 21.7 \text{ V} = 48.3 \text{ V}.$$

24. (a) By the loop rule, it remains the same. This question is aimed at student conceptualization of voltage; many students apparently confuse the concepts of voltage and current and speak of “voltage going through” a resistor – which would be difficult to rectify with the conclusion of this problem.

(b) The loop rule still applies, of course, but (by the junction rule and Ohm’s law) the voltages across R_1 and R_3 (which were the same when the switch was open) are no longer equal. More current is now being supplied by the battery which means more current is in R_3 , implying its voltage-drop has increased (in magnitude). Thus, by the loop rule (since the battery voltage has not changed) the voltage across R_1 has decreased a corresponding amount. When the switch was open, the voltage across R_1 was 6.0 V (easily seen from symmetry considerations). With the switch closed, R_1 and R_2 are equivalent (by Eq. 27-24) to $3.0\ \Omega$, which means the total load on the battery is $9.0\ \Omega$. The current therefore is 1.33 A which implies the voltage-drop across R_3 is 8.0 V. The loop rule then tells us that voltage-drop across R_1 is $12\ \text{V} - 8.0\ \text{V} = 4.0\ \text{V}$. This is a decrease of 2.0 volts from the value it had when the switch was open.

25. The voltage difference across R_3 is $V_3 = \mathcal{E}R'/(R' + 2.00\ \Omega)$, where

$$R' = (5.00\ \Omega R)/(5.00\ \Omega + R_3).$$

Thus,

$$\begin{aligned} P_3 &= \frac{V_3^2}{R_3} = \frac{1}{R_3} \left(\frac{\mathcal{E}R'}{R' + 2.00\ \Omega} \right)^2 = \frac{1}{R_3} \left(\frac{\mathcal{E}}{1 + 2.00\ \Omega/R'} \right)^2 = \frac{\mathcal{E}^2}{R_3} \left[1 + \frac{(2.00\ \Omega)(5.00\ \Omega + R)}{(5.00\ \Omega)R_3} \right]^{-2} \\ &\equiv \frac{\mathcal{E}^2}{f(R_3)} \end{aligned}$$

where we use the equivalence symbol \equiv to define the expression $f(R_3)$. To maximize P_3 we need to minimize the expression $f(R_3)$. We set

$$\frac{df(R_3)}{dR_3} = -\frac{4.00\ \Omega^2}{R_3^2} + \frac{49}{25} = 0$$

to obtain $R_3 = \sqrt{(4.00\ \Omega^2)(25)/49} = 1.43\ \Omega$.

26. (a) The voltage across $R_3 = 6.0 \, \Omega$ is $V_3 = iR_3 = (6.0 \, \text{A})(6.0 \, \Omega) = 36 \, \text{V}$. Now, the voltage across $R_1 = 2.0 \, \Omega$ is

$$(V_A - V_B) - V_3 = 78 - 36 = 42 \, \text{V},$$

which implies the current is $i_1 = (42 \, \text{V})/(2.0 \, \Omega) = 21 \, \text{A}$. By the junction rule, then, the current in $R_2 = 4.0 \, \Omega$ is $i_2 = i_1 - i = 21 - 6.0 = 15 \, \text{A}$. The total power dissipated by the resistors is (using Eq. 26-27)

$$i_1^2 (2.0 \, \Omega) + i_2^2 (4.0 \, \Omega) + i^2 (6.0 \, \Omega) = 1998 \, \text{W} \approx 2.0 \, \text{kW}.$$

By contrast, the power supplied (externally) to this section is $P_A = i_A (V_A - V_B)$ where $i_A = i_1 = 21 \, \text{A}$. Thus, $P_A = 1638 \, \text{W}$. Therefore, the "Box" must be providing energy.

(b) The rate of supplying energy is $(1998 - 1638) \, \text{W} = 3.6 \times 10^2 \, \text{W}$.

27. (a) We note that the R_1 resistors occur in series pairs, contributing net resistance $2R_1$ in each branch where they appear. Since $\mathcal{E}_2 = \mathcal{E}_3$ and $R_2 = 2R_1$, from symmetry we know that the currents through \mathcal{E}_2 and \mathcal{E}_3 are the same: $i_2 = i_3 = i$. Therefore, the current through \mathcal{E}_1 is $i_1 = 2i$. Then from $V_b - V_a = \mathcal{E}_2 - iR_2 = \mathcal{E}_1 + (2R_1)(2i)$ we get

$$i = \frac{\mathcal{E}_2 - \mathcal{E}_1}{4R_1 + R_2} = \frac{4.0 \text{ V} - 2.0 \text{ V}}{4(1.0 \, \Omega) + 2.0 \, \Omega} = 0.33 \text{ A}.$$

Therefore, the current through \mathcal{E}_1 is $i_1 = 2i = 0.67 \text{ A}$.

(b) The direction of i_1 is downward.

(c) The current through \mathcal{E}_2 is $i_2 = 0.33 \text{ A}$.

(d) The direction of i_2 is upward.

(e) From part (a), we have $i_3 = i_2 = 0.33 \text{ A}$.

(f) The direction of i_3 is also upward.

(g) $V_a - V_b = -iR_2 + \mathcal{E}_2 = -(0.333 \text{ A})(2.0 \, \Omega) + 4.0 \text{ V} = 3.3 \text{ V}$.

28. (a) For typing convenience, we denote the emf of battery 2 as V_2 and the emf of battery 1 as V_1 . The loop rule (examining the left-hand loop) gives $V_2 + i_1 R_1 - V_1 = 0$. Since V_1 is held constant while V_2 and i_1 vary, we see that this expression (for large enough V_2) will result in a negative value for i_1 – so the downward sloping line (the line that is dashed in Fig. 27-41(b)) must represent i_1 . It appears to be zero when $V_2 = 6$ V. With $i_1 = 0$, our loop rule gives $V_1 = V_2$ which implies that $V_1 = 6.0$ V.

(b) At $V_2 = 2$ V (in the graph) it appears that $i_1 = 0.2$ A. Now our loop rule equation (with the conclusion about V_1 found in part (a)) gives $R_1 = 20 \Omega$.

(c) Looking at the point where the upward-sloping i_2 line crosses the axis (at $V_2 = 4$ V), we note that $i_1 = 0.1$ A there and that the loop rule around the right-hand loop should give

$$V_1 - i_1 R_1 = i_1 R_2 \quad \text{when } i_1 = 0.1 \text{ A and } i_2 = 0.$$

This leads directly to $R_2 = 40 \Omega$.

29. Let the resistors be divided into groups of n resistors each, with all the resistors in the same group connected in series. Suppose there are m such groups that are connected in parallel with each other. Let R be the resistance of any one of the resistors. Then the equivalent resistance of any group is nR , and R_{eq} , the equivalent resistance of the whole array, satisfies

$$\frac{1}{R_{\text{eq}}} = \sum_1^m \frac{1}{nR} = \frac{m}{nR}.$$

Since the problem requires $R_{\text{eq}} = 10 \, \Omega = R$, we must select $n = m$. Next we make use of Eq. 27-16. We note that the current is the same in every resistor and there are $n \cdot m = n^2$ resistors, so the maximum total power that can be dissipated is $P_{\text{total}} = n^2 P$, where $P = 1.0 \, \text{W}$ is the maximum power that can be dissipated by any one of the resistors. The problem demands $P_{\text{total}} \geq 5.0P$, so n^2 must be at least as large as 5.0. Since n must be an integer, the smallest it can be is 3. The least number of resistors is $n^2 = 9$.

30. (a) R_2 , R_3 and R_4 are in parallel. By finding a common denominator and simplifying, the equation $1/R = 1/R_2 + 1/R_3 + 1/R_4$ gives an equivalent resistance of

$$R = \frac{R_2 R_3 R_4}{R_2 R_3 + R_2 R_4 + R_3 R_4} = \frac{(50.0\Omega)(50.0\Omega)(75.0\Omega)}{(50.0\Omega)(50.0\Omega) + (50.0\Omega)(75.0\Omega) + (50.0\Omega)(75.0\Omega)} \\ = 18.8\Omega.$$

Thus, considering the series contribution of resistor R_1 , the equivalent resistance for the network is $R_{\text{eq}} = R_1 + R = 100\Omega + 18.8\Omega = 118.8\Omega \approx 119\Omega$.

$$(b) i_1 = \mathcal{E}/R_{\text{eq}} = 6.0\text{ V}/(118.8\Omega) = 5.05 \times 10^{-2}\text{ A}.$$

$$(c) i_2 = (\mathcal{E} - V_1)/R_2 = (\mathcal{E} - i_1 R_1)/R_2 = [6.0\text{ V} - (5.05 \times 10^{-2}\text{ A})(100\Omega)]/50\Omega = 1.90 \times 10^{-2}\text{ A}.$$

$$(d) i_3 = (\mathcal{E} - V_1)/R_3 = i_2 R_2/R_3 = (1.90 \times 10^{-2}\text{ A})(50.0\Omega/50.0\Omega) = 1.90 \times 10^{-2}\text{ A}.$$

$$(e) i_4 = i_1 - i_2 - i_3 = 5.05 \times 10^{-2}\text{ A} - 2(1.90 \times 10^{-2}\text{ A}) = 1.25 \times 10^{-2}\text{ A}.$$

31. (a) The batteries are identical and, because they are connected in parallel, the potential differences across them are the same. This means the currents in them are the same. Let i be the current in either battery and take it to be positive to the left. According to the junction rule the current in R is $2i$ and it is positive to the right. The loop rule applied to either loop containing a battery and R yields

$$\mathcal{E} - ir - 2iR = 0 \Rightarrow i = \frac{\mathcal{E}}{r + 2R}.$$

The power dissipated in R is

$$P = (2i)^2 R = \frac{4\mathcal{E}^2 R}{(r + 2R)^2}.$$

We find the maximum by setting the derivative with respect to R equal to zero. The derivative is

$$\frac{dP}{dR} = \frac{4\mathcal{E}^2}{(r + 2R)^3} - \frac{16\mathcal{E}^2 R}{(r + 2R)^3} = \frac{4\mathcal{E}^2(r - 2R)}{(r + 2R)^3}.$$

The derivative vanishes (and P is a maximum) if $R = r/2$. With $r = 0.300 \, \Omega$, we have $R = 0.150 \, \Omega$.

(b) We substitute $R = r/2$ into $P = 4\mathcal{E}^2 R / (r + 2R)^2$ to obtain

$$P_{\max} = \frac{4\mathcal{E}^2(r/2)}{[r + 2(r/2)]^2} = \frac{\mathcal{E}^2}{2r} = \frac{(12.0 \, \text{V})^2}{2(0.300 \, \Omega)} = 240 \, \text{W}.$$

32. (a) By symmetry, when the two batteries are connected in parallel the current i going through either one is the same. So from $\mathcal{E} = ir + (2i)R$ with $r = 0.200\ \Omega$ and $R = 2.00r$, we get

$$i_R = 2i = \frac{2\mathcal{E}}{r + 2R} = \frac{2(12.0\text{V})}{0.200\Omega + 2(0.400\Omega)} = 24.0\ \text{A}.$$

(b) When connected in series $2\mathcal{E} - i_R r - i_R r - i_R R = 0$, or $i_R = 2\mathcal{E}/(2r + R)$.

$$i_R = 2i = \frac{2\mathcal{E}}{2r + R} = \frac{2(12.0\text{V})}{2(0.200\Omega) + 0.400\Omega} = 30.0\ \text{A}.$$

(c) In series, since $R > r$.

(d) If $R = r/2.00$, then for parallel connection,

$$i_R = 2i = \frac{2\mathcal{E}}{r + 2R} = \frac{2(12.0\text{V})}{0.200\Omega + 2(0.100\Omega)} = 60.0\ \text{A}.$$

(e) For series connection, we have

$$i_R = 2i = \frac{2\mathcal{E}}{2r + R} = \frac{2(12.0\text{V})}{2(0.200\Omega) + 0.100\Omega} = 48.0\ \text{A}.$$

(f) In parallel, since $R < r$.

33. (a) We first find the currents. Let i_1 be the current in R_1 and take it to be positive if it is to the right. Let i_2 be the current in R_2 and take it to be positive if it is to the left. Let i_3 be the current in R_3 and take it to be positive if it is upward. The junction rule produces

$$i_1 + i_2 + i_3 = 0.$$

The loop rule applied to the left-hand loop produces

$$\mathcal{E}_1 - i_1 R_1 + i_3 R_3 = 0$$

and applied to the right-hand loop produces

$$\mathcal{E}_2 - i_2 R_2 + i_3 R_3 = 0.$$

We substitute $i_3 = -i_2 - i_1$, from the first equation, into the other two to obtain

$$\mathcal{E}_1 - i_1 R_1 - i_2 R_3 - i_1 R_3 = 0$$

and

$$\mathcal{E}_2 - i_2 R_2 - i_2 R_3 - i_1 R_3 = 0.$$

Solving the above equations yield

$$i_1 = \frac{\mathcal{E}_1(R_2 + R_3) - \mathcal{E}_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} = \frac{(3.00 \text{ V})(2.00 \Omega + 5.00 \Omega) - (1.00 \text{ V})(5.00 \Omega)}{(4.00 \Omega)(2.00 \Omega) + (4.00 \Omega)(5.00 \Omega) + (2.00 \Omega)(5.00 \Omega)} = 0.421 \text{ A}.$$

$$i_2 = \frac{\mathcal{E}_2(R_1 + R_3) - \mathcal{E}_1 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} = \frac{(1.00 \text{ V})(4.00 \Omega + 5.00 \Omega) - (3.00 \text{ V})(5.00 \Omega)}{(4.00 \Omega)(2.00 \Omega) + (4.00 \Omega)(5.00 \Omega) + (2.00 \Omega)(5.00 \Omega)} = -0.158 \text{ A}.$$

$$i_3 = -\frac{\mathcal{E}_2 R_1 + \mathcal{E}_1 R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} = -\frac{(1.00 \text{ V})(4.00 \Omega) + (3.00 \text{ V})(2.00 \Omega)}{(4.00 \Omega)(2.00 \Omega) + (4.00 \Omega)(5.00 \Omega) + (2.00 \Omega)(5.00 \Omega)} = -0.263 \text{ A}.$$

Note that the current i_3 in R_3 is actually downward and the current i_2 in R_2 is to the right. The current i_1 in R_1 is to the right.

(a) The power dissipated in R_1 is $P_1 = i_1^2 R_1 = (0.421 \text{ A})^2 (4.00 \Omega) = 0.709 \text{ W}$.

(b) The power dissipated in R_2 is $P_2 = i_2^2 R_2 = (-0.158 \text{ A})^2 (2.00 \Omega) = 0.0499 \text{ W} \approx 0.050 \text{ W}$.

(c) The power dissipated in R_3 is $P_3 = i_3^2 R_3 = (-0.263 \text{ A})^2 (5.00 \Omega) = 0.346 \text{ W}$.

(d) The power supplied by \mathcal{E}_1 is $i_3 \mathcal{E}_1 = (0.421 \text{ A})(3.00 \text{ V}) = 1.26 \text{ W}$.

(e) The power “supplied” by \mathcal{E}_2 is $i_2 \mathcal{E}_2 = (-0.158 \text{ A})(1.00 \text{ V}) = -0.158 \text{ W}$. The negative sign indicates that \mathcal{E}_2 is actually absorbing energy from the circuit.

34. (a) When $R_3 = 0$ all the current passes through R_1 and R_3 and avoids R_2 altogether. Since that value of the current (through the battery) is 0.006 A (see Fig. 27-45(b)) for $R_3 = 0$ then (using Ohm's law) $R_1 = (12 \text{ V})/(0.006 \text{ A}) = 2.0 \times 10^3 \Omega$.

(b) When $R_3 = \infty$ all the current passes through R_1 and R_2 and avoids R_3 altogether. Since that value of the current (through the battery) is 0.002 A (stated in problem) for $R_3 = \infty$ then (using Ohm's law) $R_2 = (12 \text{ V})/(0.002 \text{ A}) - R_1 = 4.0 \times 10^3 \Omega$.

35. (a) The copper wire and the aluminum sheath are connected in parallel, so the potential difference is the same for them. Since the potential difference is the product of the current and the resistance, $i_C R_C = i_A R_A$, where i_C is the current in the copper, i_A is the current in the aluminum, R_C is the resistance of the copper, and R_A is the resistance of the aluminum. The resistance of either component is given by $R = \rho L/A$, where ρ is the resistivity, L is the length, and A is the cross-sectional area. The resistance of the copper wire is $R_C = \rho_C L/\pi a^2$, and the resistance of the aluminum sheath is $R_A = \rho_A L/\pi(b^2 - a^2)$. We substitute these expressions into $i_C R_C = i_A R_A$, and cancel the common factors L and π to obtain

$$\frac{i_C \rho_C}{a^2} = \frac{i_A \rho_A}{b^2 - a^2}.$$

We solve this equation simultaneously with $i = i_C + i_A$, where i is the total current. We find

$$i_C = \frac{r_C^2 \rho_C i}{(r_A^2 - r_C^2) \rho_C + r_C^2 \rho_A}$$

and

$$i_A = \frac{(r_A^2 - r_C^2) \rho_C i}{(r_A^2 - r_C^2) \rho_C + r_C^2 \rho_A}.$$

The denominators are the same and each has the value

$$\begin{aligned} (b^2 - a^2) \rho_C + a^2 \rho_A &= \left[(0.380 \times 10^{-3} \text{ m})^2 - (0.250 \times 10^{-3} \text{ m})^2 \right] (1.69 \times 10^{-8} \Omega \cdot \text{m}) \\ &\quad + (0.250 \times 10^{-3} \text{ m})^2 (2.75 \times 10^{-8} \Omega \cdot \text{m}) \\ &= 3.10 \times 10^{-15} \Omega \cdot \text{m}^3. \end{aligned}$$

Thus,

$$i_C = \frac{(0.250 \times 10^{-3} \text{ m})^2 (2.75 \times 10^{-8} \Omega \cdot \text{m}) (2.00 \text{ A})}{3.10 \times 10^{-15} \Omega \cdot \text{m}^3} = 1.11 \text{ A}$$

(b) and

$$i_A = \frac{\left[(0.380 \times 10^{-3} \text{ m})^2 - (0.250 \times 10^{-3} \text{ m})^2 \right] (1.69 \times 10^{-8} \Omega \cdot \text{m}) (2.00 \text{ A})}{3.10 \times 10^{-15} \Omega \cdot \text{m}^3} = 0.893 \text{ A}.$$

(c) Consider the copper wire. If V is the potential difference, then the current is given by $V = i_C R_C = i_C \rho_C L / \pi a^2$, so

$$L = \frac{\pi a^2 V}{i_C \rho_C} = \frac{(\pi)(0.250 \times 10^{-3} \text{ m})^2 (12.0 \text{ V})}{(1.11 \text{ A})(1.69 \times 10^{-8} \Omega \cdot \text{m})} = 126 \text{ m}.$$

36. (a) We use $P = \mathcal{E}^2/R_{\text{eq}}$, where

$$R_{\text{eq}} = 7.00 \, \Omega + \frac{(12.0 \, \Omega)(4.00 \, \Omega) R}{(12.0 \, \Omega)(4.00 \, \Omega) + (12.0 \, \Omega) R + (4.00 \, \Omega) R}.$$

Put $P = 60.0 \, \text{W}$ and $\mathcal{E} = 24.0 \, \text{V}$ and solve for R : $R = 19.5 \, \Omega$.

(b) Since $P \propto R_{\text{eq}}$, we must minimize R_{eq} , which means $R = 0$.

(c) Now we must maximize R_{eq} , or set $R = \infty$.

(d) Since $R_{\text{eq, min}} = 7.00 \, \Omega$, $P_{\text{max}} = \mathcal{E}^2/R_{\text{eq, min}} = (24.0 \, \text{V})^2/7.00 \, \Omega = 82.3 \, \text{W}$.

(e) Since

$$R_{\text{eq, max}} = 7.00 \, \Omega + (12.0 \, \Omega)(4.00 \, \Omega)/(12.0 \, \Omega + 4.00 \, \Omega) = 10.0 \, \Omega,$$

$$P_{\text{min}} = \mathcal{E}^2/R_{\text{eq, max}} = (24.0 \, \text{V})^2/10.0 \, \Omega = 57.6 \, \text{W}.$$

37. (a) The current in R_1 is given by

$$i_1 = \frac{\mathcal{E}}{R_1 + R_2 R_3 / (R_2 + R_3)} = \frac{5.0 \text{ V}}{2.0 \Omega + (4.0 \Omega)(6.0 \Omega) / (4.0 \Omega + 6.0 \Omega)} = 1.14 \text{ A}.$$

Thus

$$i_3 = \frac{\mathcal{E} - V_1}{R_3} = \frac{\mathcal{E} - i_1 R_1}{R_3} = \frac{5.0 \text{ V} - (1.14 \text{ A})(2.0 \Omega)}{6.0 \Omega} = 0.45 \text{ A}.$$

(b) We simply interchange subscripts 1 and 3 in the equation above. Now

$$i_3 = \frac{\mathcal{E}}{R_3 + (R_2 R_1 / (R_2 + R_1))} = \frac{5.0 \text{ V}}{6.0 \Omega + ((2.0 \Omega)(4.0 \Omega) / (2.0 \Omega + 4.0 \Omega))} = 0.6818 \text{ A}$$

and

$$i_1 = \frac{5.0 \text{ V} - (0.6818 \text{ A})(6.0 \Omega)}{2.0 \Omega} = 0.45 \text{ A},$$

the same as before.

38. (a) Since $i = \mathcal{E}/(r + R_{\text{ext}})$ and $i_{\text{max}} = \mathcal{E}/r$, we have $R_{\text{ext}} = R(i_{\text{max}}/i - 1)$ where $r = 1.50 \text{ V}/1.00 \text{ mA} = 1.50 \times 10^3 \text{ } \Omega$. Thus,

$$R_{\text{ext}} = (1.5 \times 10^3 \text{ } \Omega) (1/0.100 - 1) = 1.35 \times 10^4 \text{ } \Omega.$$

(b) $R_{\text{ext}} = (1.5 \times 10^3 \text{ } \Omega) (1/0.500 - 1) = 1.50 \times 10^3 \text{ } \Omega$.

(c) $R_{\text{ext}} = (1.5 \times 10^3 \text{ } \Omega) (1/0.900 - 1) = 167 \text{ } \Omega$.

(d) Since $r = 20.0 \text{ } \Omega + R$, $R = 1.50 \times 10^3 \text{ } \Omega - 20.0 \text{ } \Omega = 1.48 \times 10^3 \text{ } \Omega$.

39. The current in R_2 is i . Let i_1 be the current in R_1 and take it to be downward. According to the junction rule the current in the voltmeter is $i - i_1$ and it is downward. We apply the loop rule to the left-hand loop to obtain

$$\mathcal{E} - iR_2 - i_1 R_1 - ir = 0.$$

We apply the loop rule to the right-hand loop to obtain

$$i_1 R_1 - (i - i_1) R_V = 0.$$

The second equation yields

$$i = \frac{R_1 + R_V}{R_V} i_1.$$

We substitute this into the first equation to obtain

$$\mathcal{E} - \frac{(R_2 + r)(R_1 + R_V)}{R_V} i_1 + R_1 i_1 = 0.$$

This has the solution

$$i_1 = \frac{\mathcal{E} R_V}{(R_2 + r)(R_1 + R_V) + R_1 R_V}.$$

The reading on the voltmeter is

$$\begin{aligned} i_1 R_1 &= \frac{\mathcal{E} R_V R_1}{(R_2 + r)(R_1 + R_V) + R_1 R_V} = \frac{(3.0\text{V})(5.0 \times 10^3 \Omega)(250 \Omega)}{(300 \Omega + 100 \Omega)(250 \Omega + 5.0 \times 10^3 \Omega) + (250 \Omega)(5.0 \times 10^3 \Omega)} \\ &= 1.12\text{V}. \end{aligned}$$

The current in the absence of the voltmeter can be obtained by taking the limit as R_V becomes infinitely large. Then

$$i_1 R_1 = \frac{\mathcal{E} R_1}{R_1 + R_2 + r} = \frac{(3.0\text{V})(250 \Omega)}{250 \Omega + 300 \Omega + 100 \Omega} = 1.15\text{V}.$$

The fractional error is $(1.12 - 1.15)/(1.15) = -0.030$, or -3.0% .

40. (a) $\mathcal{E} = V + ir = 12 \text{ V} + (10.0 \text{ A})(0.0500 \Omega) = 12.5 \text{ V}.$

(b) Now $\mathcal{E} = V' + (i_{\text{motor}} + 8.00 \text{ A})r$, where $V' = i_A' R_{\text{light}} = (8.00 \text{ A})(12.0 \text{ V}/10 \text{ A}) = 9.60 \text{ V}.$ Therefore,

$$i_{\text{motor}} = \frac{\mathcal{E} - V'}{r} - 8.00 \text{ A} = \frac{12.5 \text{ V} - 9.60 \text{ V}}{0.0500 \Omega} - 8.00 \text{ A} = 50.0 \text{ A}.$$

41. Since the current in the ammeter is i , the voltmeter reading is $V' = V + i R_A = i (R + R_A)$, or $R = V'/i - R_A = R' - R_A$, where $R' = V'/i$ is the apparent reading of the resistance.

Now, from the lower loop of the circuit diagram, the current through the voltmeter is $i_V = \mathcal{E} / (R_{\text{eq}} + R_0)$, where

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_V} + \frac{1}{R_A + R} \Rightarrow R_{\text{eq}} = \frac{R_V (R + R_A)}{R_V + R + R_A} = \frac{(300 \Omega)(85.0 \Omega + 3.00 \Omega)}{300 \Omega + 85.0 \Omega + 3.00 \Omega} = 68.0 \Omega.$$

The voltmeter reading is then

$$V' = i_V R_{\text{eq}} = \frac{\mathcal{E} R_{\text{eq}}}{R_{\text{eq}} + R_0} = \frac{(12.0 \text{ V})(68.0 \Omega)}{68.0 \Omega + 100 \Omega} = 4.86 \text{ V}.$$

(a) The ammeter reading is

$$i = \frac{V'}{R + R_A} = \frac{4.86 \text{ V}}{85.0 \Omega + 3.00 \Omega} = 0.0552 \text{ A}.$$

(b) As shown above, the voltmeter reading is $V' = 4.86 \text{ V}$.

(c) $R' = V'/i = 4.86 \text{ V} / (5.52 \times 10^{-2} \text{ A}) = 88.0 \Omega$.

(d) Since $R = R' - R_A$, if R_A is decreased, the difference between R' and R decreases. In fact, when $R_A = 0$, $R' = R$.

42. The currents in R and R_V are i and $i' - i$, respectively. Since $V = iR = (i' - i)R_V$ we have, by dividing both sides by V , $1 = (i'/V - i/V)R_V = (1/R' - 1/R)R_V$. Thus,

$$\frac{1}{R} = \frac{1}{R'} - \frac{1}{R_V} \Rightarrow R' = \frac{RR_V}{R + R_V}.$$

The equivalent resistance of the circuit is $R_{\text{eq}} = R_A + R_0 + R' = R_A + R_0 + \frac{RR_V}{R + R_V}$.

(a) The ammeter reading is

$$i' = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{\mathcal{E}}{R_A + R_0 + R_V R/(R + R_V)} = \frac{12.0 \text{ V}}{3.00 \Omega + 100 \Omega + (300 \Omega)(85.0 \Omega)/(300 \Omega + 85.0 \Omega)} \\ = 7.09 \times 10^{-2} \text{ A}.$$

(b) The voltmeter reading is

$$V = \mathcal{E} - i'(R_A + R_0) = 12.0 \text{ V} - (0.0709 \text{ A})(103.00 \Omega) = 4.70 \text{ V}.$$

(c) The apparent resistance is $R' = V/i' = 4.70 \text{ V}/(7.09 \times 10^{-2} \text{ A}) = 66.3 \Omega$.

(d) If R_V is increased, the difference between R and R' decreases. In fact, $R' \rightarrow R$ as $R_V \rightarrow \infty$.

43. Let i_1 be the current in R_1 and R_2 , and take it to be positive if it is toward point a in R_1 . Let i_2 be the current in R_s and R_x , and take it to be positive if it is toward b in R_s . The loop rule yields $(R_1 + R_2)i_1 - (R_x + R_s)i_2 = 0$. Since points a and b are at the same potential, $i_1 R_1 = i_2 R_s$. The second equation gives $i_2 = i_1 R_1 / R_s$, which is substituted into the first equation to obtain

$$(R_1 + R_2)i_1 = (R_x + R_s)\frac{R_1}{R_s}i_1 \Rightarrow R_x = \frac{R_2 R_s}{R_1}.$$

44. (a) We use $q = q_0 e^{-t/\tau}$, or $t = \tau \ln (q_0/q)$, where $\tau = RC$ is the capacitive time constant. Thus, $t_{1/3} = \tau \ln [q_0/(2q_0/3)] = \tau \ln (3/2) = 0.41 \tau$, or $t_{1/3}/\tau = 0.41$.

(b) $t_{2/3} = \tau \ln [q_0/(q_0/3)] = \tau \ln 3 = 1.1 \tau$, or $t_{2/3}/\tau = 1.1$.

45. During charging, the charge on the positive plate of the capacitor is given by

$$q = C\mathcal{E}(1 - e^{-t/\tau}),$$

where C is the capacitance, \mathcal{E} is applied emf, and $\tau = RC$ is the capacitive time constant. The equilibrium charge is $q_{\text{eq}} = C\mathcal{E}$. We require $q = 0.99q_{\text{eq}} = 0.99C\mathcal{E}$, so

$$0.99 = 1 - e^{-t/\tau}.$$

Thus, $e^{-t/\tau} = 0.01$. Taking the natural logarithm of both sides, we obtain $t/\tau = -\ln 0.01 = 4.61$ or $t = 4.61\tau$.

46. (a) $\tau = RC = (1.40 \times 10^6 \Omega)(1.80 \times 10^{-6} \text{ F}) = 2.52 \text{ s}.$

(b) $q_o = \mathcal{E}C = (12.0 \text{ V})(1.80 \mu\text{ F}) = 21.6 \mu\text{C}.$

(c) The time t satisfies $q = q_o(1 - e^{-t/RC})$, or

$$t = RC \ln \left(\frac{q_o}{q_o - q} \right) = (2.52 \text{ s}) \ln \left(\frac{21.6 \mu\text{C}}{21.6 \mu\text{C} - 16.0 \mu\text{C}} \right) = 3.40 \text{ s}.$$

47. (a) The voltage difference V across the capacitor is $V(t) = \mathcal{E}(1 - e^{-t/RC})$. At $t = 1.30 \mu\text{s}$ we have $V(t) = 5.00 \text{ V}$, so $5.00 \text{ V} = (12.0 \text{ V})(1 - e^{-1.30 \mu\text{s}/RC})$, which gives

$$\tau = (1.30 \mu\text{s})/\ln(12/7) = 2.41 \mu\text{s}.$$

(b) $C = \tau/R = 2.41 \mu\text{s}/15.0 \text{ k}\Omega = 161 \text{ pF}$.

48. Here we denote the battery emf as V . Then the requirement stated in the problem that the resistor voltage be equal to the capacitor voltage becomes $iR = V_{\text{cap}}$, or

$$Ve^{-t/RC} = V(1 - e^{-t/RC})$$

where Eqs. 27-34 and 27-35 have been used. This leads to $t = RC \ln 2$, or $t = 0.208 \text{ ms}$.

49. (a) The potential difference V across the plates of a capacitor is related to the charge q on the positive plate by $V = q/C$, where C is capacitance. Since the charge on a discharging capacitor is given by $q = q_0 e^{-t/\tau}$, this means $V = V_0 e^{-t/\tau}$ where V_0 is the initial potential difference. We solve for the time constant τ by dividing by V_0 and taking the natural logarithm:

$$\tau = -\frac{t}{\ln(V/V_0)} = -\frac{10.0 \text{ s}}{\ln[(1.00 \text{ V})/(100 \text{ V})]} = 2.17 \text{ s}.$$

(b) At $t = 17.0 \text{ s}$, $t/\tau = (17.0 \text{ s})/(2.17 \text{ s}) = 7.83$, so

$$V = V_0 e^{-t/\tau} = (100 \text{ V})e^{-7.83} = 3.96 \times 10^{-2} \text{ V}.$$

50. The potential difference across the capacitor varies as a function of time t as $V(t) = V_0 e^{-t/RC}$. Using $V = V_0/4$ at $t = 2.0$ s, we find

$$R = \frac{t}{C \ln(V_0/V)} = \frac{2.0 \text{ s}}{(2.0 \times 10^{-6} \text{ F}) \ln 4} = 7.2 \times 10^5 \Omega.$$

51. (a) The initial energy stored in a capacitor is given by $U_C = q_0^2 / 2C$, where C is the capacitance and q_0 is the initial charge on one plate. Thus

$$q_0 = \sqrt{2CU_C} = \sqrt{2(1.0 \times 10^{-6} \text{ F})(0.50 \text{ J})} = 1.0 \times 10^{-3} \text{ C} .$$

(b) The charge as a function of time is given by $q = q_0 e^{-t/\tau}$, where τ is the capacitive time constant. The current is the derivative of the charge

$$i = -\frac{dq}{dt} = \frac{q_0}{\tau} e^{-t/\tau} ,$$

and the initial current is $i_0 = q_0 / \tau$. The time constant is

$$\tau = RC = (1.0 \times 10^{-6} \text{ F})(1.0 \times 10^6 \Omega) = 1.0 \text{ s} .$$

Thus $i_0 = (1.0 \times 10^{-3} \text{ C}) / (1.0 \text{ s}) = 1.0 \times 10^{-3} \text{ A} .$

(c) We substitute $q = q_0 e^{-t/\tau}$ into $V_C = q/C$ to obtain

$$V_C = \frac{q_0}{C} e^{-t/\tau} = \left(\frac{1.0 \times 10^{-3} \text{ C}}{1.0 \times 10^{-6} \text{ F}} \right) e^{-t/1.0 \text{ s}} = (1.0 \times 10^3 \text{ V}) e^{-1.0t} ,$$

where t is measured in seconds.

(d) We substitute $i = (q_0 / \tau) e^{-t/\tau}$ into $V_R = iR$ to obtain

$$V_R = \frac{q_0 R}{\tau} e^{-t/\tau} = \frac{(1.0 \times 10^{-3} \text{ C})(1.0 \times 10^6 \Omega)}{1.0 \text{ s}} e^{-t/1.0 \text{ s}} = (1.0 \times 10^3 \text{ V}) e^{-1.0t} ,$$

where t is measured in seconds.

(e) We substitute $i = (q_0 / \tau) e^{-t/\tau}$ into $P = i^2 R$ to obtain

$$P = \frac{q_0^2 R}{\tau^2} e^{-2t/\tau} = \frac{(1.0 \times 10^{-3} \text{ C})^2 (1.0 \times 10^6 \Omega)}{(1.0 \text{ s})^2} e^{-2t/1.0 \text{ s}} = (1.0 \text{ W}) e^{-2.0t} ,$$

where t is again measured in seconds.

52. The time it takes for the voltage difference across the capacitor to reach V_L is given by $V_L = \mathcal{E}(1 - e^{-t/RC})$. We solve for R :

$$R = \frac{t}{C \ln[\mathcal{E}/(\mathcal{E} - V_L)]} = \frac{0.500 \text{ s}}{(0.150 \times 10^{-6} \text{ F}) \ln[95.0 \text{ V}/(95.0 \text{ V} - 72.0 \text{ V})]} = 2.35 \times 10^6 \Omega$$

where we used $t = 0.500 \text{ s}$ given (implicitly) in the problem.

53. At $t = 0$ the capacitor is completely uncharged and the current in the capacitor branch is as it would be if the capacitor were replaced by a wire. Let i_1 be the current in R_1 and take it to be positive if it is to the right. Let i_2 be the current in R_2 and take it to be positive if it is downward. Let i_3 be the current in R_3 and take it to be positive if it is downward. The junction rule produces $i_1 = i_2 + i_3$, the loop rule applied to the left-hand loop produces

$$\mathcal{E} - i_1 R_1 - i_2 R_2 = 0 ,$$

and the loop rule applied to the right-hand loop produces

$$i_2 R_2 - i_3 R_3 = 0 .$$

Since the resistances are all the same we can simplify the mathematics by replacing R_1 , R_2 , and R_3 with R .

(a) Solving the three simultaneous equations, we find

$$i_1 = \frac{2\mathcal{E}}{3R} = \frac{2(1.2 \times 10^3 \text{ V})}{3(0.73 \times 10^6 \Omega)} = 1.1 \times 10^{-3} \text{ A}$$

$$(b) i_2 = \frac{\mathcal{E}}{3R} = \frac{1.2 \times 10^3 \text{ V}}{3(0.73 \times 10^6 \Omega)} = 5.5 \times 10^{-4} \text{ A}.$$

$$(c) i_3 = i_2 = 5.5 \times 10^{-4} \text{ A}.$$

At $t = \infty$ the capacitor is fully charged and the current in the capacitor branch is 0. Thus, $i_1 = i_2$, and the loop rule yields

$$\mathcal{E} - i_1 R_1 - i_1 R_2 = 0 .$$

(d) The solution is

$$i_1 = \frac{\mathcal{E}}{2R} = \frac{1.2 \times 10^3 \text{ V}}{2(0.73 \times 10^6 \Omega)} = 8.2 \times 10^{-4} \text{ A}.$$

$$(e) i_2 = i_1 = 8.2 \times 10^{-4} \text{ A}.$$

(f) As stated before, the current in the capacitor branch is $i_3 = 0$.

We take the upper plate of the capacitor to be positive. This is consistent with current flowing into that plate. The junction equation is $i_1 = i_2 + i_3$, and the loop equations are

$$\mathcal{E} - i_1 R - i_2 R = 0 \quad \text{and} \quad -\frac{q}{C} - i_3 R + i_2 R = 0 .$$

We use the first equation to substitute for i_1 in the second and obtain $\mathcal{E} - 2i_2 R - i_3 R = 0$. Thus $i_2 = (\mathcal{E} - i_3 R)/2R$. We substitute this expression into the third equation above to obtain $-(q/C) - (i_3 R) + (\mathcal{E}/2) - (i_3 R/2) = 0$. Now we replace i_3 with dq/dt to obtain

$$\frac{3R}{2} \frac{dq}{dt} + \frac{q}{C} = \frac{\mathcal{E}}{2} .$$

This is just like the equation for an RC series circuit, except that the time constant is $\tau = 3RC/2$ and the impressed potential difference is $\mathcal{E}/2$. The solution is

$$q = \frac{C\mathcal{E}}{2} (1 - e^{-2t/3RC}) .$$

The current in the capacitor branch is

$$i_3(t) = \frac{dq}{dt} = \frac{\mathcal{E}}{3R} e^{-2t/3RC} .$$

The current in the center branch is

$$i_2(t) = \frac{\mathcal{E}}{2R} - \frac{i_3}{2} = \frac{\mathcal{E}}{2R} - \frac{\mathcal{E}}{6R} e^{-2t/3RC} = \frac{\mathcal{E}}{6R} (3 - e^{-2t/3RC})$$


and the potential difference across R_2 is

$$V_2(t) = i_2 R = \frac{\mathcal{E}}{6} (3 - e^{-2t/3RC}) .$$

(g) For $t = 0$, $e^{-2t/3RC}$ is 1 and $V_2 = \mathcal{E}/3 = (1.2 \times 10^3 \text{ V})/3 = 4.0 \times 10^2 \text{ V}$.

(h) For $t = \infty$, $e^{-2t/3RC}$ is 0 and $V_2 = \mathcal{E}/2 = (1.2 \times 10^3 \text{ V})/2 = 6.0 \times 10^2 \text{ V}$.

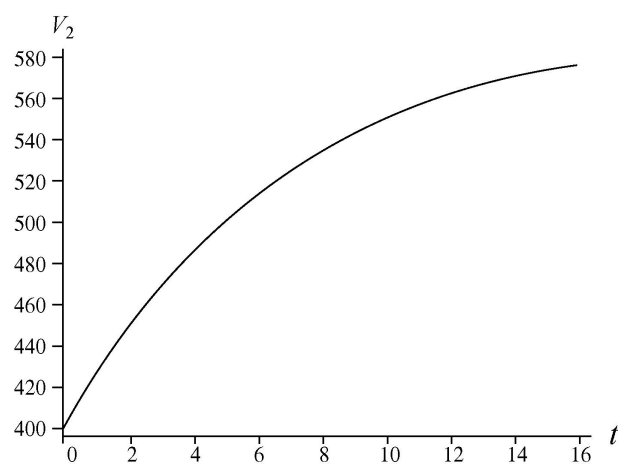(i) A plot of V_2 as a function of time is shown in the following graph.



54. In the steady state situation, the capacitor voltage will equal the voltage across $R_2 =$

15 k Ω :

$$V_0 = R_2 \frac{\mathcal{E}}{R_1 + R_2} = (15.0 \text{ k}\Omega) \left(\frac{20.0 \text{ V}}{10.0 \text{ k}\Omega + 15.0 \text{ k}\Omega} \right) = 12.0 \text{ V}.$$

Now, multiplying Eq. 27-39 by the capacitance leads to $V = V_0 e^{-t/RC}$ describing the voltage across the capacitor (and across $R_2 = 15.0 \text{ k}\Omega$) after the switch is opened (at $t = 0$). Thus, with $t = 0.00400 \text{ s}$, we obtain

$$V = (12) e^{-0.004 / (15000)(0.4 \times 10^{-6})} = 6.16 \text{ V}.$$

Therefore, using Ohm's law, the current through R_2 is $6.16 / 15000 = 4.11 \times 10^{-4} \text{ A}$.

55. (a) The charge on the positive plate of the capacitor is given by

$$q = C\mathcal{E}(1 - e^{-t/\tau}),$$

where \mathcal{E} is the emf of the battery, C is the capacitance, and τ is the time constant. The value of τ is

$$\tau = RC = (3.00 \times 10^6 \Omega)(1.00 \times 10^{-6} \text{ F}) = 3.00 \text{ s}.$$

At $t = 1.00 \text{ s}$, $t/\tau = (1.00 \text{ s})/(3.00 \text{ s}) = 0.333$ and the rate at which the charge is increasing is

$$\frac{dq}{dt} = \frac{C\mathcal{E}}{\tau} e^{-t/\tau} = \frac{(1.00 \times 10^{-6})(4.00 \text{ V})}{3.00 \text{ s}} e^{-0.333} = 9.55 \times 10^{-7} \text{ C/s}.$$

(b) The energy stored in the capacitor is given by $U_c = \frac{q^2}{2C}$, and its rate of change is

$$\frac{dU_c}{dt} = \frac{q}{C} \frac{dq}{dt}.$$

Now

$$q = C\mathcal{E}(1 - e^{-t/\tau}) = (1.00 \times 10^{-6})(4.00 \text{ V})(1 - e^{-0.333}) = 1.13 \times 10^{-6} \text{ C},$$

so

$$\frac{dU_c}{dt} = \left(\frac{1.13 \times 10^{-6} \text{ C}}{1.00 \times 10^{-6} \text{ F}} \right) (9.55 \times 10^{-7} \text{ C/s}) = 1.08 \times 10^{-6} \text{ W}.$$

(c) The rate at which energy is being dissipated in the resistor is given by $P = i^2 R$. The current is $9.55 \times 10^{-7} \text{ A}$, so

$$P = (9.55 \times 10^{-7} \text{ A})^2 (3.00 \times 10^6 \Omega) = 2.74 \times 10^{-6} \text{ W}.$$

(d) The rate at which energy is delivered by the battery is

$$i\mathcal{E} = (9.55 \times 10^{-7} \text{ A})(4.00 \text{ V}) = 3.82 \times 10^{-6} \text{ W}.$$

The energy delivered by the battery is either stored in the capacitor or dissipated in the resistor. Conservation of energy requires that $i\varepsilon = (q/C) (dq/dt) + i^2R$. Except for some round-off error the numerical results support the conservation principle.

56. We apply Eq. 27-39 to each capacitor, demand their initial charges are in a ratio of 3:2 as described in the problem, and solve for the time: we obtain

$$t = \frac{\ln\left(\frac{3}{2}\right)}{\left(\frac{1}{R_2 C_2} - \frac{1}{R_1 C_1}\right)} = 162 \mu\text{s} .$$

57. We use the result of problem 50: $R = t/[C \ln(V_0/V)]$.

(a) Then, for $t_{\min} = 10.0 \mu\text{s}$

$$R_{\min} = \frac{10.0 \mu\text{s}}{(0.220 \mu\text{F}) \ln(5.00/0.800)} = 24.8 \Omega.$$

(b) For $t_{\max} = 6.00 \text{ ms}$,

$$R_{\max} = \left(\frac{6.00 \text{ ms}}{10.0 \mu\text{s}} \right) (24.8 \Omega) = 1.49 \times 10^4 \Omega ,$$

where in the last equation we used $\tau = RC$.

58. (a) We denote $L = 10$ km and $\alpha = 13$ Ω/km . Measured from the east end we have

$$R_1 = 100 \Omega = 2\alpha(L - x) + R,$$

and measured from the west end $R_2 = 200 \Omega = 2\alpha x + R$. Thus,

$$x = \frac{R_2 - R_1}{4\alpha} + \frac{L}{2} = \frac{200\Omega - 100\Omega}{4(13\Omega/\text{km})} + \frac{10\text{ km}}{2} = 6.9 \text{ km}.$$

(b) Also, we obtain

$$R = \frac{R_1 + R_2}{2} - \alpha L = \frac{100\Omega + 200\Omega}{2} - (13\Omega/\text{km})(10\text{ km}) = 20\Omega.$$

59. (a) From symmetry we see that the current through the top set of batteries (i) is the same as the current through the second set. This implies that the current through the $R = 4.0\ \Omega$ resistor at the bottom is $i_R = 2i$. Thus, with r denoting the internal resistance of each battery (equal to $4.0\ \Omega$) and \mathcal{E} denoting the 20 V emf, we consider one loop equation (the outer loop), proceeding counterclockwise:

$$3(\mathcal{E} - ir) - (2i)R = 0.$$

This yields $i = 3.0\ \text{A}$. Consequently, $i_R = 6.0\ \text{A}$.

(b) The terminal voltage of each battery is $\mathcal{E} - ir = 8.0\ \text{V}$.

(c) Using Eq. 27-17, we obtain $P = i\mathcal{E} = (3)(20) = 60\ \text{W}$.

(d) Using Eq. 26-27, we have $P = i^2r = 36\ \text{W}$.

60. The equivalent resistance in Fig. 27-59 (with n parallel resistors) is

$$R_{\text{eq}} = R + \frac{R}{n} = \frac{(n+1)R}{n}.$$

The current in the battery in this case should be $i_n = \frac{V_{\text{battery}}}{R_{\text{eq}}} = \frac{n V_{\text{battery}}}{(n+1)R}$. If there were $n+1$ parallel resistors, then

$$i_{n+1} = \frac{(n+1)V_{\text{battery}}}{(n+2)R}.$$

For the relative increase to be 0.0125 ($= 1/80$), we require

$$\frac{i_{n+1} - i_n}{i_n} = \frac{i_{n+1}}{i_n} - 1 = \frac{\left(\frac{n+1}{n+2}\right)}{\left(\frac{n}{n+1}\right)} - 1 = \frac{1}{80}.$$

This leads to the second-degree equation $n^2 + 2n - 80 = (n+10)(n-8) = 0$. Clearly the only physically interesting solution to this is $n = 8$. Thus, there are eight resistors in parallel (as well as that resistor in series shown towards the bottom) in Fig. 27-59.

61. (a) The magnitude of the current density vector is

$$J_A = \frac{i}{A} = \frac{V}{(R_1 + R_2)A} = \frac{4V}{(R_1 + R_2)\pi D^2} = \frac{4(60.0\text{ V})}{\pi(0.127\,\Omega + 0.729\,\Omega)(2.60 \times 10^{-3}\text{ m})^2} \\ = 1.32 \times 10^7 \text{ A/m}^2.$$

(b) $V_A = V R_1 / (R_1 + R_2) = (60.0\text{ V})(0.127\,\Omega) / (0.127\,\Omega + 0.729\,\Omega) = 8.90\text{ V},$

(c) The resistivity for A is

$$\rho_A = R_A A / L_A = \pi R_A D^2 / 4 L_A = \pi(0.127\,\Omega)(2.60 \times 10^{-3}\text{ m})^2 / [4(40.0\text{ m})] = 1.69 \times 10^{-8}\,\Omega \cdot \text{m}.$$

So A is made of copper.

(d) $J_B = J_A = 1.32 \times 10^7 \text{ A/m}^2.$

(e) $V_B = V - V_A = 60.0\text{ V} - 8.9\text{ V} = 51.1\text{ V}.$

(f) The resistivity for B is $\rho_B = 9.68 \times 10^{-8}\,\Omega \cdot \text{m},$ so B is made of iron.

62. Line 1 has slope $R_1 = 6 \text{ k}\Omega$. Line 2 has slope $R_2 = 4 \text{ k}\Omega$. Line 3 has slope $R_3 = 2 \text{ k}\Omega$. The parallel pair equivalence is $R_{12} = R_1 R_2 / (R_1 + R_2) = 2.4 \text{ k}\Omega$. That in series with R_3 gives an equivalence of $4.4 \text{ k}\Omega$. The current through the battery is therefore $(6 \text{ V}) / (4.4 \text{ k}\Omega)$ and the voltage drop across R_3 is $(6 \text{ V})(2 \text{ k}\Omega) / (4.4 \text{ k}\Omega) = 2.73 \text{ V}$. Subtracting this (because of the loop rule) from the battery voltage leaves us with the voltage across R_2 . Then Ohm's law gives the current through R_2 : $(6 \text{ V} - 2.73 \text{ V}) / (4 \text{ k}\Omega) = 0.82 \text{ mA}$

63. (a) Since $R_{\text{tank}} = 140\ \Omega$, $i = 12\text{ V} / (10\ \Omega + 140\ \Omega) = 8.0 \times 10^{-2}\text{ A}$.

(b) Now, $R_{\text{tank}} = (140\ \Omega + 20\ \Omega)/2 = 80\ \Omega$, so $i = 12\text{ V} / (10\ \Omega + 80\ \Omega) = 0.13\text{ A}$.

(c) When full, $R_{\text{tank}} = 20\ \Omega$ so $i = 12\text{ V} / (10\ \Omega + 20\ \Omega) = 0.40\text{ A}$.

64. (a) The loop rule leads to a voltage-drop across resistor 3 equal to 5.0 V (since the total drop along the upper branch must be 12 V). The current there is consequently $i = (5.0 \text{ V})/(200 \, \Omega) = 25 \text{ mA}$. Then the resistance of resistor 1 must be $(2.0 \text{ V})/i = 80 \, \Omega$.

(b) Resistor 2 has the same voltage-drop as resistor 3; its resistance is $200 \, \Omega$, also.

65. (a) Here we denote the battery emf as V . See Fig. 27-4(a): $V_T = V - ir$.

(b) Doing a least squares fit for the V_T versus i values listed, we obtain

$$V_T = 13.61 - 0.0599i$$

which implies $V = 13.6$ volts.

(c) It also implies the internal resistance is $0.060\ \Omega$.

66. (a) The loop rule (proceeding counterclockwise around the right loop) leads to $\mathcal{E}_2 - i_1 R_1 = 0$ (where i_1 was assumed downward). This yields $i_1 = 0.0600$ A.

(b) The direction of i_1 is downward.

(c) The loop rule (counterclockwise around the left loop) gives

$$(+\mathcal{E}_1) + (+i_1 R_1) + (-i_2 R_2) = 0$$

where i_2 has been assumed leftward. This yields $i_3 = 0.180$ A.

(d) A positive value of i_3 implies that our assumption on the direction is correct, i.e., it flows leftward.

(e) The junction rule tells us that the current through the 12 V battery is $0.180 + 0.0600 = 0.240$ A.

(f) The direction is upward.

67. (a) The charge q on the capacitor as a function of time is $q(t) = (\mathcal{E}C)(1 - e^{-t/RC})$, so the charging current is $i(t) = dq/dt = (\mathcal{E}/R)e^{-t/RC}$. The energy supplied by the emf is then

$$U = \int_0^{\infty} \mathcal{E} i \, dt = \frac{\mathcal{E}^2}{R} \int_0^{\infty} e^{-t/RC} \, dt = C\mathcal{E}^2 = 2U_C$$

where $U_C = \frac{1}{2}C\mathcal{E}^2$ is the energy stored in the capacitor.

(b) By directly integrating $i^2 R$ we obtain

$$U_R = \int_0^{\infty} i^2 R \, dt = \frac{\mathcal{E}^2}{R} \int_0^{\infty} e^{-2t/RC} \, dt = \frac{1}{2}C\mathcal{E}^2.$$

68. (a) Using Eq. 27-4, we take the derivative of the power $P = i^2 R$ with respect to R and set the result equal to zero:

$$\frac{dP}{dR} = \frac{d}{dR} \left(\frac{\mathcal{E}^2 R}{(R+r)^2} \right) = \frac{\mathcal{E}^2 (r-R)}{(R+r)^3} = 0$$

which clearly has the solution $R = r$.

(b) When $R = r$, the power dissipated in the external resistor equals

$$P_{\max} = \left. \frac{\mathcal{E}^2 R}{(R+r)^2} \right|_{R=r} = \frac{\mathcal{E}^2}{4r}.$$

69. Here we denote the battery emf as V . Eq. 27-30 leads to

$$i = \frac{V}{R} - \frac{q}{RC} = \frac{12}{4} - \frac{8}{(4)(4)} = 2.5 \text{ A} .$$

70. The equivalent resistance of the series pair of $R_3 = R_4 = 2.0 \, \Omega$ is $R_{34} = 4.0 \, \Omega$, and the equivalent resistance of the parallel pair of $R_1 = R_2 = 4.0 \, \Omega$ is $R_{12} = 2.0 \, \Omega$. Since the voltage across R_{34} must equal that across R_{12} :

$$V_{34} = V_{12} \Rightarrow i_{34} R_{34} = i_{12} R_{12} \Rightarrow i_{34} = \frac{1}{2} i_{12}$$

This relation, plus the junction rule condition $I = i_{12} + i_{34} = 6.00 \, \text{A}$ leads to the solution $i_{12} = 4.0 \, \text{A}$. It is clear by symmetry that $i_1 = i_{12} / 2 = 2.00 \, \text{A}$.

71. (a) The work done by the battery relates to the potential energy change:

$$q\Delta V = eV = e(12.0\text{ V}) = 12.0\text{ eV}.$$

(b) $P = iV = neV = (3.40 \times 10^{18}/\text{s})(1.60 \times 10^{-19}\text{ C})(12.0\text{ V}) = 6.53\text{ W}.$

72. (a) Since $P = \mathcal{E}^2/R_{\text{eq}}$, the higher the power rating the smaller the value of R_{eq} . To achieve this, we can let the low position connect to the larger resistance (R_1), middle position connect to the smaller resistance (R_2), and the high position connect to both of them in parallel.

(b) For $P = 300 \text{ W}$, $R_{\text{eq}} = R_1 R_2 / (R_1 + R_2) = (144 \text{ } \Omega) R_2 / (144 \text{ } \Omega + R_2) = (120 \text{ V})^2 / 300 \text{ W}$. We obtain $R_2 = 72 \text{ } \Omega$.

(c) For $P = 100 \text{ W}$, $R_{\text{eq}} = R_1 = \mathcal{E}^2 / P = (120 \text{ V})^2 / 100 \text{ W} = 144 \text{ } \Omega$;

73. The internal resistance of the battery is $r = (12 \text{ V} - 11.4 \text{ V})/50 \text{ A} = 0.012 \text{ } \Omega < 0.020 \text{ } \Omega$, so the battery is OK. The resistance of the cable is

$$R = 3.0 \text{ V}/50 \text{ A} = 0.060 \text{ } \Omega > 0.040 \text{ } \Omega,$$

so the cable is defective.

74. (a) If S_1 is closed, and S_2 and S_3 are open, then $i_a = \mathcal{E}/2R_1 = 120 \text{ V}/40.0 \, \Omega = 3.00 \text{ A}$.

(b) If S_3 is open while S_1 and S_2 remain closed, then

$$R_{\text{eq}} = R_1 + R_1 (R_1 + R_2) / (2R_1 + R_2) = 20.0 \, \Omega + (20.0 \, \Omega) \times (30.0 \, \Omega) / (50.0 \, \Omega) = 32.0 \, \Omega,$$

so $i_a = \mathcal{E}/R_{\text{eq}} = 120 \text{ V}/32.0 \, \Omega = 3.75 \text{ A}$.

(c) If all three switches S_1 , S_2 and S_3 are closed, then $R_{\text{eq}} = R_1 + R_1 R' / (R_1 + R')$ where

$$R' = R_2 + R_1 (R_1 + R_2) / (2R_1 + R_2) = 22.0 \, \Omega,$$

i.e.,

$$R_{\text{eq}} = 20.0 \, \Omega + (20.0 \, \Omega) (22.0 \, \Omega) / (20.0 \, \Omega + 22.0 \, \Omega) = 30.5 \, \Omega,$$

so $i_a = \mathcal{E}/R_{\text{eq}} = 120 \text{ V}/30.5 \, \Omega = 3.94 \text{ A}$.

75. (a) Reducing the bottom two series resistors to a single $R' = 4.00 \, \Omega$ (with current i_1 through it), we see we can make a path (for use with the loop rule) that passes through R , the $\mathcal{E}_4 = 5.00 \, \text{V}$ battery, the $\mathcal{E}_1 = 20.0 \, \text{V}$ battery, and the $\mathcal{E}_3 = 5.00 \, \text{V}$. This leads to

$$i_1 = \frac{\mathcal{E}_1 + \mathcal{E}_3 + \mathcal{E}_4}{4.0 \, \Omega} = \frac{30.0 \, \text{V}}{4.0 \, \Omega} = 7.50 \, \text{A}.$$

(b) The direction of i_1 is leftward.

(c) The voltage across the bottom series pair is $i_1 R' = 30.0 \, \text{V}$. This must be the same as the voltage across the two resistors directly above them, one of which has current i_2 through it and the other (by symmetry) has current $\frac{1}{2} i_2$ through it. Therefore,

$$30.0 \, \text{V} = i_2 (2.00 \, \Omega) + \frac{1}{2} i_2 (2.00 \, \Omega)$$

leads to $i_2 = 10.0 \, \text{A}$.

(d) The direction of i_2 is also leftward.

(e) We use Eq. 27-17: $P_4 = (i_1 + i_2) \mathcal{E}_4 = 87.5 \, \text{W}$.

(f) The energy is being supplied to the circuit since the current is in the "forward" direction through the battery.

76. The bottom two resistors are in parallel, equivalent to a $2.0R$ resistance. This, then, is in series with resistor R on the right, so that their equivalence is $R' = 3.0R$. Now, near the top left are two resistors ($2.0R$ and $4.0R$) which are in series, equivalent to $R'' = 6.0R$. Finally, R' and R'' are in parallel, so the net equivalence is

$$R_{\text{eq}} = \frac{(R')(R'')}{R' + R''} = 2.0R = 20 \, \Omega$$

where in the final step we use the fact that $R = 10 \, \Omega$.

77. (a) The four resistors R_1 , R_2 , R_3 and R_4 on the left reduce to

$$R_{\text{eq}} = R_{12} + R_{34} = \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4} = 7.0\Omega + 3.0\Omega = 10\Omega$$

With $\mathcal{E} = 30 \text{ V}$ across R_{eq} the current there is $i_2 = 3.0 \text{ A}$.

(b) The three resistors on the right reduce to

$$R'_{\text{eq}} = R_{56} + R_7 = \frac{R_5 R_6}{R_5 + R_6} + R_7 = \frac{(6.0\Omega)(2.0\Omega)}{6.0\Omega + 2.0\Omega} + 1.5\Omega = 3.0\Omega.$$

With $\mathcal{E} = 30 \text{ V}$ across R'_{eq} the current there is $i_4 = 10 \text{ A}$.

(c) By the junction rule, $i_1 = i_2 + i_4 = 13 \text{ A}$.

(d) By symmetry, $i_3 = \frac{1}{2} i_2 = 1.5 \text{ A}$.

(e) By the loop rule (proceeding clockwise),

$$30\text{V} - i_4(1.5 \Omega) - i_5(2.0 \Omega) = 0$$

readily yields $i_5 = 7.5 \text{ A}$.

78. (a) We analyze the lower left loop and find $i_1 = \mathcal{E}_1/R = (12.0 \text{ V})/(4.00 \text{ } \Omega) = 3.00 \text{ A}$.

(b) The direction of i_1 is downward.

(c) Letting $R = 4.00 \text{ } \Omega$, we apply the loop rule to the tall rectangular loop in the center of the figure (proceeding clockwise):

$$\mathcal{E}_2 + (+i_1 R) + (-i_2 R) + \left(-\frac{i_2}{2} R\right) + (-i_2 R) = 0 \text{ .}$$

Using the result from part (a), we find $i_2 = 1.60 \text{ A}$.

(d) The direction of i_2 is downward (as was assumed in writing the equation as we did).

(e) Battery 1 is supplying this power since the current is in the "forward" direction through the battery.

(f) We apply Eq. 27-17: The current through the $\mathcal{E}_1 = 12.0 \text{ V}$ battery is, by the junction rule, $1.60 + 3.00 = 4.60 \text{ A}$ and $P = (4.60)(12.0 \text{ V}) = 55.2 \text{ W}$.

(g) Battery 2 is supplying this power since the current is in the "forward" direction through the battery.

(h) $P = i_2(4.00 \text{ V}) = 6.40 \text{ W}$.

79. (a) We reduce the parallel pair of resistors (at the bottom of the figure) to a single $R' = 1.00 \, \Omega$ resistor and then reduce it with its series 'partner' (at the lower left of the figure) to obtain an equivalence of $R'' = 2.00 \, \Omega + 1.00 \, \Omega = 3.00 \, \Omega$. It is clear that the current through R'' is the i_1 we are solving for. Now, we employ the loop rule, choose a path that includes R'' and all the batteries (proceeding clockwise). Thus, assuming i_1 goes leftward through R'' , we have

$$5.00 \, \text{V} + 20.0 \, \text{V} - 10.0 \, \text{V} - i_1 R'' = 0$$

which yields $i_1 = 5.00 \, \text{A}$.

(b) Since i_1 is positive, our assumption regarding its direction (leftward) was correct.

(c) Since the current through the $\mathcal{E}_1 = 20.0 \, \text{V}$ battery is "forward", battery 1 is supplying energy.

(d) The rate is $P_1 = (5.00 \, \text{A})(20.0 \, \text{V}) = 100 \, \text{W}$.

(e) Reducing the parallel pair (which are in parallel to the $\mathcal{E}_2 = 10.0 \, \text{V}$ battery) to a single $R' = 1.00 \, \Omega$ resistor (and thus with current $i' = (10.0 \, \text{V})/(1.00 \, \Omega) = 10.0 \, \text{A}$ downward through it), we see that the current through the battery (by the junction rule) must be $i = i' - i_1 = 5.00 \, \text{A}$ *upward* (which is the "forward" direction for that battery). Thus, battery 2 is supplying energy.

(f) Using Eq. 27-17, we obtain $P_2 = 50.0 \, \text{W}$.

(g) The set of resistors that are in parallel with the $\mathcal{E}_3 = 5 \, \text{V}$ battery is reduced to $R''' = 0.800 \, \Omega$ (accounting for the fact that two of those resistors are actually reduced in series, first, before the parallel reduction is made), which has current $i''' = (5.00 \, \text{V})/(0.800 \, \Omega) = 6.25 \, \text{A}$ downward through it. Thus, the current through the battery (by the junction rule) must be $i = i''' + i_1 = 11.25 \, \text{A}$ *upward* (which is the "forward" direction for that battery). Thus, battery 3 is supplying energy.

(h) Eq. 27-17 leads to $P_3 = 56.3 \, \text{W}$.

80. (a) The parallel set of three identical $R_2 = 18\ \Omega$ resistors reduce to $R = 6.0\ \Omega$, which is now in series with the $R_1 = 6.0\ \Omega$ resistor at the top right, so that the total resistive load across the battery is $R' = R_1 + R = 12\ \Omega$. Thus, the current through R' is $(12\text{V})/R' = 1.0\ \text{A}$, which is the current through R . By symmetry, we see one-third of that passes through any one of those $18\ \Omega$ resistors; therefore, $i_1 = 0.333\ \text{A}$.

(b) The direction of i_1 is clearly rightward.

(c) We use Eq. 26-27: $P = i^2 R' = (1.0)^2(12) = 12\ \text{W}$. Thus, in 60 s, the energy dissipated is $(12\ \text{J/s})(60\ \text{s}) = 720\ \text{J}$.

81. We denote silicon with subscript s and iron with i . Let $T_0 = 20^\circ$. If

$$\begin{aligned} R(T) &= R_s(T) + R_i(T) = R_s(T_0)[1 + \alpha(T - T_0)] + R_i(T_0)[1 + \alpha_i(T - T_0)] \\ &= (R_s(T_0)\alpha_s + R_i(T_0)\alpha_i) + (\text{temperature independent terms}) \end{aligned}$$

is to be temperature-independent, we must require that $R_s(T_0)\alpha_s + R_i(T_0)\alpha_i = 0$. Also note that $R_s(T_0) + R_i(T_0) = R = 1000 \Omega$. We solve for $R_s(T_0)$ and $R_i(T_0)$ to obtain

$$R_s(T_0) = \frac{R\alpha_i}{\alpha_i - \alpha_s} = \frac{(1000\Omega)(6.5 \times 10^{-3})}{6.5 \times 10^{-3} - 70 \times 10^{-3}} = 85.0\Omega.$$

(b) $R_i(T_0) = 1000 \Omega - 85.0 \Omega = 915 \Omega.$

82. (a) Since $R_{\text{eq}} < R$, the two resistors ($R = 12.0 \, \Omega$ and R_x) must be connected in parallel:

$$R_{\text{eq}} = 3.00 \, \Omega = \frac{R_x R}{R + R_x} = \frac{R_x (12.0 \, \Omega)}{12.0 \, \Omega + R_x}.$$

We solve for R_x : $R_x = R_{\text{eq}} R / (R - R_{\text{eq}}) = (3.00 \, \Omega)(12.0 \, \Omega) / (12.0 \, \Omega - 3.00 \, \Omega) = 4.00 \, \Omega$.

(b) As stated above, the resistors must be connected in parallel.

83. Consider the lowest branch with the two resistors $R_4 = 3.00\ \Omega$ and $R_5 = 5.00\ \Omega$. The voltage difference across R_5 is

$$V = i_5 R_5 = \frac{\mathcal{E} R_5}{R_4 + R_5} = \frac{(120\text{ V})(5.00\ \Omega)}{3.00\ \Omega + 5.00\ \Omega} = 7.50\text{ V}.$$

84. When connected in series, the rate at which electric energy dissipates is $P_s = \mathcal{E}^2/(R_1 + R_2)$. When connected in parallel, the corresponding rate is $P_p = \mathcal{E}^2(R_1 + R_2)/R_1R_2$. Letting $P_p/P_s = 5$, we get $(R_1 + R_2)^2/R_1R_2 = 5$, where $R_1 = 100 \, \Omega$. We solve for R_2 : $R_2 = 38 \, \Omega$ or $260 \, \Omega$.

(a) Thus, the smaller value of R_2 is $38 \, \Omega$.

(b) The larger value of R_2 is $260 \, \Omega$.

85. (a) We reduce the parallel pair of identical $2.0\ \Omega$ resistors (on the right side) to $R' = 1.0\ \Omega$, and we reduce the series pair of identical $2.0\ \Omega$ resistors (on the upper left side) to $R'' = 4.0\ \Omega$. With R denoting the $2.0\ \Omega$ resistor at the bottom (between V_2 and V_1), we now have three resistors in series which are equivalent to

$$R + R' + R'' = 7.0\ \Omega$$

across which the voltage is $7.0\ \text{V}$ (by the loop rule, this is $12\ \text{V} - 5.0\ \text{V}$), implying that the current is $1.0\ \text{A}$ (clockwise). Thus, the voltage across R' is $(1.0\ \text{A})(1.0\ \Omega) = 1.0\ \text{V}$, which means that (examining the right side of the circuit) the voltage difference between *ground* and V_1 is $12 - 1 = 11\ \text{V}$. Noting the orientation of the battery, we conclude $V_1 = -11\ \text{V}$.

(b) The voltage across R'' is $(1.0\ \text{A})(4.0\ \Omega) = 4.0\ \text{V}$, which means that (examining the left side of the circuit) the voltage difference between *ground* and V_2 is $5.0 + 4.0 = 9.0\ \text{V}$. Noting the orientation of the battery, we conclude $V_2 = -9.0\ \text{V}$. This can be verified by considering the voltage across R and the value we obtained for V_1 .

86. (a) From $P = V^2/R$ we find $V = \sqrt{PR} = \sqrt{(10\text{ W})(0.10\,\Omega)} = 1.0\text{ V}.$

(b) From $i = V/R = (\mathcal{E} - V)/r$ we find

$$r = R\left(\frac{\mathcal{E} - V}{V}\right) = (0.10\,\Omega)\left(\frac{1.5\text{ V} - 1.0\text{ V}}{1.0\text{ V}}\right) = 0.050\,\Omega.$$

87. (a) $R_{\text{eq}}(AB) = 20.0 \, \Omega / 3 = 6.67 \, \Omega$ (three $20.0 \, \Omega$ resistors in parallel).

(b) $R_{\text{eq}}(AC) = 20.0 \, \Omega / 3 = 6.67 \, \Omega$ (three $20.0 \, \Omega$ resistors in parallel).

(c) $R_{\text{eq}}(BC) = 0$ (as B and C are connected by a conducting wire).

88. Note that there is no voltage drop across the ammeter. Thus, the currents in the bottom resistors are the same, which we call i (so the current through the battery is $2i$ and the voltage drop across each of the bottom resistors is iR). The resistor network can be reduced to an equivalence of

$$R_{\text{eq}} = \frac{(2R)(R)}{2R + R} + \frac{(R)(R)}{R + R} = \frac{7}{6}R$$

which means that we can determine the current through the battery (and also through each of the bottom resistors):

$$2i = \frac{\mathcal{E}}{R_{\text{eq}}} \Rightarrow i = \frac{3\mathcal{E}}{7R}.$$

By the loop rule (going around the left loop, which includes the battery, resistor $2R$ and one of the bottom resistors), we have

$$\mathcal{E} - i_{2R}(2R) - iR = 0 \Rightarrow i_{2R} = \frac{\mathcal{E} - iR}{2R}.$$

Substituting $i = 3\mathcal{E}/7R$, this gives $i_{2R} = 2\mathcal{E}/7R$. The difference between i_{2R} and i is the current through the ammeter. Thus,

$$i_{\text{ammeter}} = i - i_{2R} = \frac{3\mathcal{E}}{7R} - \frac{2\mathcal{E}}{7R} = \frac{\mathcal{E}}{7R} \Rightarrow \frac{i_{\text{ammeter}}}{\mathcal{E}/R} = \frac{1}{7} = 0.143.$$

89. When S is open for a long time, the charge on C is $q_i = \mathcal{E}_2 C$. When S is closed for a long time, the current i in R_1 and R_2 is

$$i = (\mathcal{E}_2 - \mathcal{E}_1)/(R_1 + R_2) = (3.0 \text{ V} - 1.0 \text{ V})/(0.20 \, \Omega + 0.40 \, \Omega) = 3.33 \text{ A}.$$

The voltage difference V across the capacitor is then

$$V = \mathcal{E}_2 - iR_2 = 3.0 \text{ V} - (3.33 \text{ A})(0.40 \, \Omega) = 1.67 \text{ V}.$$

Thus the final charge on C is $q_f = VC$. So the change in the charge on the capacitor is

$$\Delta q = q_f - q_i = (V - \mathcal{E}_2)C = (1.67 \text{ V} - 3.0 \text{ V})(10 \, \mu\text{F}) = -13 \, \mu\text{C}.$$

90. Using the junction and the loop rules, we have

$$20.0 - i_1 R_1 - i_3 R_3 = 0$$

$$20.0 - i_1 R_1 - i_2 R_2 - 50 = 0$$

$$i_2 + i_3 = i_1$$

Requiring no current through the battery 1 means that $i_1=0$, or $i_2 = i_3$. Solving the above equations with $R_1=10.0\Omega$ and $R_2=20.0\Omega$, we obtain

$$i_1 = \frac{40 - 3R_3}{20 + 3R_3} = 0 \Rightarrow R_3 = \frac{40}{3} = 13.3\Omega$$

91. (a) The capacitor is *initially* uncharged, which implies (by the loop rule) that there is zero voltage (at $t = 0$) across the $R_2 = 10 \text{ k}\Omega$ resistor, and that 30 V is across the $R_1 = 20 \text{ k}\Omega$ resistor. Therefore, by Ohm's law, $i_{10} = (30 \text{ V})/(20 \text{ k}\Omega) = 1.5 \times 10^{-3} \text{ A}$.

(b) $i_{20} = 0$,

(c) As $t \rightarrow \infty$ the current to the capacitor reduces to zero and the $20 \text{ k}\Omega$ and $10 \text{ k}\Omega$ resistors behave more like a series pair (having the same current), equivalent to $30 \text{ k}\Omega$. The current through them, then, at long times, is

$$i = (30 \text{ V})/(30 \text{ k}\Omega) = 1.0 \times 10^{-3} \text{ A}.$$

92. (a) The six resistors to the left of $\mathcal{E}_1 = 16 \text{ V}$ battery can be reduced to a single resistor $R = 8.0 \, \Omega$, through which the current must be $i_R = \mathcal{E}_1/R = 2.0 \text{ A}$. Now, by the loop rule, the current through the $3.0 \, \Omega$ and $1.0 \, \Omega$ resistors at the upper right corner is

$$i' = \frac{16.0 \text{ V} - 8.0 \text{ V}}{3.0 \, \Omega + 1.0 \, \Omega} = 2.0 \text{ A}$$

in a direction that is “backward” relative to the $\mathcal{E}_2 = 8.0 \text{ V}$ battery. Thus, by the junction rule,

$$i_1 = i_R + i' = 4.0 \text{ A} .$$

(b) The direction of i_1 is upward (that is, in the “forward” direction relative to \mathcal{E}_1).

(c) The current i_2 derives from a succession of symmetric splittings of i_R (reversing the procedure of reducing those six resistors to find R in part (a)). We find

$$i_2 = \frac{1}{2} \left(\frac{1}{2} i_R \right) = 0.50 \text{ A} .$$

(d) The direction of i_2 is clearly downward.

(e) Using our conclusion from part (a) in Eq. 27-17, we have $P = i_1 \mathcal{E}_1 = (4.0)(16) = 64 \text{ W}$.

(f) Using results from part (a) in Eq. 27-17, we obtain $P = i' \mathcal{E}_2 = (2.0)(8.0) = 16 \text{ W}$.

(g) Energy is being supplied in battery 1.

(h) Energy is being absorbed in battery 2.

93. With the unit Ω understood, the equivalent resistance for this circuit is

$$R_{\text{eq}} = \frac{20R_3 + 100}{R_3 + 10}.$$

Therefore, the power supplied by the battery (equal to the power dissipated in the resistors) is

$$P = \frac{V^2}{R_3} = V^2 \frac{R_3 + 10}{20R_3 + 100}$$

where $V = 12$ V. We attempt to extremize the expression by working through the $dP/dR_3 = 0$ condition and do not find a value of R_3 that satisfies it.

(a) We note, then, that the function is a monotonically decreasing function of R_3 , with $R_3 = 0$ giving the maximum possible value (since $R_3 < 0$ values are not being allowed).

(b) With the value $R_3 = 0$, we obtain $P = 14.4$ W.

94. (a) The symmetry of the problem allows us to use i_2 as the current in *both* of the R_2 resistors and i_1 for the R_1 resistors. We see from the junction rule that $i_3 = i_1 - i_2$. There are only two independent loop rule equations:

$$\begin{aligned}\mathcal{E} - i_2 R_2 - i_1 R_1 &= 0 \\ \mathcal{E} - 2i_1 R_1 - (i_1 - i_2) R_3 &= 0\end{aligned}$$

where in the latter equation, a zigzag path through the bridge has been taken. Solving, we find $i_1 = 0.002625$ A, $i_2 = 0.00225$ A and $i_3 = i_1 - i_2 = 0.000375$ A. Therefore, $V_A - V_B = i_1 R_1 = 5.25$ V.

(b) It follows also that $V_B - V_C = i_3 R_3 = 1.50$ V.

(c) We find $V_C - V_D = i_1 R_1 = 5.25$ V.

(d) Finally, $V_A - V_C = i_2 R_2 = 6.75$ V.

95. (a) Using the junction rule ($i_1 = i_2 + i_3$) we write two loop rule equations:

$$\mathcal{E}_1 - i_2 R_2 - (i_2 + i_3) R_1 = 0$$

$$\mathcal{E}_2 - i_3 R_3 - (i_2 + i_3) R_1 = 0.$$

Solving, we find $i_2 = 0.0109$ A (rightward, as was assumed in writing the equations as we did), $i_3 = 0.0273$ A (leftward), and $i_1 = i_2 + i_3 = 0.0382$ A (downward).

(b) downward. See the results in part (a).

(c) $i_2 = 0.0109$ A . See the results in part (a).

(d) rightward. See the results in part (a).

(e) $i_3 = 0.0273$ A. See the results in part (a).

(f) leftward. See the results in part (a).

(g) The voltage across R_1 equals V_A : $(0.0382 \text{ A})(100 \, \Omega) = +3.82 \text{ V}$.

96. (a) R_2 and R_3 are in parallel; their equivalence is in series with R_1 . Therefore,

$$R_{\text{eq}} = R_1 + \frac{R_2 R_3}{R_2 + R_3} = 300 \, \Omega.$$

(b) The current through the battery is $\mathcal{E}/R_{\text{eq}} = 0.0200 \, \text{A}$, which is also the current through R_1 . Hence, the voltage across R_1 is $V_1 = (0.0200 \, \text{A})(100 \, \Omega) = 2.00 \, \text{V}$.

(c) From the loop rule,

$$\mathcal{E} - V_1 - i_3 R_3 = 0$$

which yields $i_3 = 6.67 \times 10^{-3} \, \text{A}$.

97. From $V_a - \mathcal{E}_1 = V_c - ir_1 - iR$ and $i = (\mathcal{E}_1 - \mathcal{E}_2)/(R + r_1 + r_2)$, we get

$$\begin{aligned} V_a - V_c &= \mathcal{E}_1 - i(r_1 + R) = \mathcal{E}_1 - \left(\frac{\mathcal{E}_1 - \mathcal{E}_2}{R + r_1 + r_2} \right) (r_1 + R) \\ &= 4.4\text{V} - \left(\frac{4.4\text{V} - 2.1\text{V}}{5.5\Omega + 1.8\Omega + 2.3\Omega} \right) (2.3\Omega + 5.5\Omega) \\ &= 2.5\text{V}. \end{aligned}$$

98. The potential difference across R_2 is

$$V_2 = iR_2 = \frac{\mathcal{E} R_2}{R_1 + R_2 + R_3} = \frac{(12 \text{ V})(4.0 \Omega)}{3.0 \Omega + 4.0 \Omega + 5.0 \Omega} = 4.0 \text{ V}.$$

99. (a) By symmetry, we see that i_3 is half the current that goes through the battery. The battery current is found by dividing \mathcal{E} by the equivalent resistance of the circuit, which is easily found to be $6.00\ \Omega$. Thus,

$$i_3 = \frac{1}{2} i_{\text{bat}} = \frac{1}{2} \left(\frac{12\text{ V}}{6.0\ \Omega} \right) = 1.00\text{ A}$$

and is clearly downward (in the figure).

(b) We use Eq. 27-17: $P = i_{\text{bat}} \mathcal{E} = 24.0\text{ W}$.

100. The current in the ammeter is given by $i_A = \mathcal{E}/(r + R_1 + R_2 + R_A)$. The current in R_1 and R_2 without the ammeter is $i = \mathcal{E}/(r + R_1 + R_2)$. The percent error is then

$$\begin{aligned}\frac{\Delta i}{i} &= \frac{i - i_A}{i} = 1 - \frac{r + R_1 + R_2}{r + R_1 + R_2 + R_A} = \frac{R_A}{r + R_1 + R_2 + R_A} \\ &= \frac{0.10\Omega}{2.0\Omega + 5.0\Omega + 4.0\Omega + 0.10\Omega} = 0.90\%.\end{aligned}$$

101. When all the batteries are connected in parallel, each supplies a current i ; thus, $i_R = Ni$. Then from $\mathcal{E} = ir + i_R R = ir + Nir$, we get $i_R = N\mathcal{E}/[(N+1)r]$. When all the batteries are connected in series, $i_r = i_R$ and

$$\mathcal{E}_{\text{total}} = N\mathcal{E} = Ni_r r + i_R R = Ni_R r + i_R R,$$

so $i_R = N\mathcal{E}/[(N+1)r]$.

102. (a) Dividing Eq. 27-39 by capacitance turns it into an equation that describes the dependence of the voltage on time: $V_C = V_0 e^{-t/\tau}$;

(b) Taking logarithms of this equation produces a form amenable to a least squares fit:

$$\ln(V_C) = -\frac{1}{\tau} t + \ln(V_0)$$

$$\ln(V_C) = -1.2994 t + 2.525$$

Thus, we have the emf equal to $V_0 = e^{2.525} = 12.49 \text{ V} \approx 12 \text{ V}$;

(c) This also tells us that the time constant is $\tau = 1/1.2994 = 0.77 \text{ s}$.

(d) Since $\tau = RC$ then we find $C = 3.8 \text{ }\mu\text{F}$.

103. Here we denote the supply emf as V (understood to be in volts). The situation is much like that shown in Fig. 27-4, with r now interpreted as the resistance of the transmission line and R interpreted as the resistance of the “consumer” (the reason the circuit has been turned on in the first place – to supply power to some resistive load R). From Eq. 27-4 and Eq. 26-27 (remembering that we are asked to find the power dissipated in the *transmission line*) we obtain

$$P_{line} = \left(\frac{V^2}{(R + r)^2} \right) r .$$

Now r is considered constant, certainly, but what about R ? The load will not be the same in the two cases (where $V = 110000$ and $V' = 110$) because the problem requires us to consider the *total* power supplied to be constant, so

$$P_{total} = \left(\frac{V^2}{(R + r)^2} \right) (R + r) = P'_{total} = \left(\frac{V'^2}{(R' + r)^2} \right) (R' + r)$$

which implies (taking ratio of P_{total} to P'_{total})

$$1 = \frac{V^2 (R' + r)}{V'^2 (R + r)} .$$

Now, as the problem directs, we take ratio of P_{line} to P'_{line} and obtain

$$\frac{P_{line}}{P'_{line}} = \frac{V^2 (R' + r)^2}{V'^2 (R + r)^2} = \frac{V'^2}{V^2} = 1.00 \times 10^{-6} .$$

104. The resistor by the letter i is above three other resistors; together, these four resistors are equivalent to a resistor $R = 10\ \Omega$ (with current i). As if we were presented with a maze, we find a path through R that passes through any number of batteries (10, it turns out) but no other resistors, which — as in any good maze — winds “all over the place.” Some of the ten batteries are opposing each other (particularly the ones along the outside), so that their net emf is only $\mathcal{E} = 40\text{ V}$.

(a) The current through R is then $i = \mathcal{E}/R = 4.0\text{ A}$.

(b) The direction is upward in the figure.

105. The maximum power output is $(120\text{ V})(15\text{ A}) = 1800\text{ W}$. Since $1800\text{ W}/500\text{ W} = 3.6$, the maximum number of 500 W lamps allowed is 3.

106. The part of R_0 connected in parallel with R is given by $R_1 = R_0x/L$, where $L = 10$ cm. The voltage difference across R is then $V_R = \mathcal{E}R'/R_{\text{eq}}$, where $R' = RR_1/(R + R_1)$ and $R_{\text{eq}} = R_0(1 - x/L) + R'$. Thus

$$P_R = \frac{V_R^2}{R} = \frac{1}{R} \left(\frac{\mathcal{E}RR_1/(R + R_1)}{R_0(1 - x/L) + RR_1/(R + R_1)} \right)^2 = \frac{100R(\mathcal{E}x/R_0)^2}{(100R/R_0 + 10x - x^2)^2},$$

where x is measured in cm.

107. The power delivered by the motor is $P = (2.00 \text{ V})(0.500 \text{ m/s}) = 1.00 \text{ W}$. From $P = i^2 R_{\text{motor}}$ and $\mathcal{E} = i(r + R_{\text{motor}})$ we then find $i^2 r - i\mathcal{E} + P = 0$ (which also follows directly from the conservation of energy principle). We solve for i :

$$i = \frac{\mathcal{E} \pm \sqrt{\mathcal{E}^2 - 4rP}}{2r} = \frac{2.00 \text{ V} \pm \sqrt{(2.00 \text{ V})^2 - 4(0.500 \Omega)(1.00 \text{ W})}}{2(0.500 \Omega)}.$$

The answer is either 3.41 A or 0.586 A.

(a) The larger i is 3.41 A.

(b) We use $V = \mathcal{E} - ir = 2.00 \text{ V} - i(0.500 \Omega)$. We substitute value of i obtained in part (a) into the above formula to get $V = 0.293 \text{ V}$.

(c) The smaller i is 0.586 A.

(d) The corresponding V is 1.71 V.

108. (a) Placing a wire (of resistance r) with current i running directly from point a to point b in Fig. 27-51 divides the top of the picture into a left and a right triangle. If we label the currents through each resistor with the corresponding subscripts (for instance, i_s goes toward the lower right through R_s and i_x goes toward the upper right through R_x), then the currents must be related as follows:

$$\begin{aligned} i_0 &= i_1 + i_s & \text{and} & & i_1 &= i + i_2 \\ i_s + i &= i_x & \text{and} & & i_2 + i_x &= i_0 \end{aligned}$$

where the last relation is not independent of the previous three. The loop equations for the two triangles and also for the bottom loop (containing the battery and point b) lead to

$$\begin{aligned} i_s R_s - i_1 R_1 - ir &= 0 \\ i_2 R_s - i_x R_x - ir &= 0 \\ \mathcal{E} - i_0 R_0 - i_s R_s - i_x R_x &= 0. \end{aligned}$$

We incorporate the current relations from above into these loop equations in order to obtain three well-posed “simultaneous” equations, for three unknown currents (i_s , i_1 and i):

$$\begin{aligned} i_s R_s - i_1 R_1 - ir &= 0 \\ i_1 R_2 - i_s R_x - i(r + R_x + R_2) &= 0 \\ \mathcal{E} - i_s(R_0 + R_s + R_x) - i_1 R_0 - i R_x &= 0 \end{aligned}$$

The problem statement further specifies $R_1 = R_2 = R$ and $R_0 = 0$, which causes our solution for i to simplify significantly. It becomes

$$i = \frac{\mathcal{E}(R_s - R_x)}{2rR_s + 2R_x R_s + R_s R + 2rR_x + R_x R}$$

which is equivalent to the result shown in the problem statement.

(b) Examining the numerator of our final result in part (a), we see that the condition for $i = 0$ is $R_s = R_x$. Since $R_1 = R_2 = R$, this is equivalent to $R_x = R_s R_2 / R_1$, consistent with the result of Problem 43.

109. (a) They are in parallel and the portions of A and B between the load and their respective sliding contacts have the same potential difference. It is clearly important not to “short” the system (particularly if the load turns out to have very little resistance) by having the sliding contacts too close to the load-ends of A and B to start with. Thus, we suggest putting the contacts roughly in the middle of each. Since $R_A > R_B$, larger currents generally go through B (depending on the position of the sliding contact) than through A . Therefore, B is analogous to a “coarse” control, as A is to a “fine control.” Hence, we recommend adjusting the current roughly with B , and then making fine adjustments with A .

(b) Relatively large percentage changes in A cause only small percentage changes in the resistance of the parallel combination, thus permitting fine adjustment; any change in A causes half as much change in this combination.

110. (a) In the process described in the problem, no charge is gained or lost. Thus, $q =$ constant. Hence,

$$q = C_1 V_1 = C_2 V_2 \Rightarrow V_2 = V_1 \frac{C_1}{C_2} = (200) \left(\frac{150}{10} \right) = 3.0 \times 10^3 \text{ V}.$$

(b) Eq. 27-39, with $\tau = RC$, describes not only the discharging of q but also of V . Thus,

$$V = V_0 e^{-t/\tau} \Rightarrow t = RC \ln \left(\frac{V_0}{V} \right) = (300 \times 10^9 \Omega) (10 \times 10^{-12} \text{ F}) \ln \left(\frac{3000}{100} \right)$$

which yields $t = 10$ s. This is a longer time than most people are inclined to wait before going on to their next task (such as handling the sensitive electronic equipment).

(c) We solve $V = V_0 e^{-t/RC}$ for R with the new values $V_0 = 1400$ V and $t = 0.30$ s. Thus,

$$R = \frac{t}{C \ln(V_0/V)} = \frac{0.30 \text{ s}}{(10 \times 10^{-12} \text{ F}) \ln(1400/100)} = 1.1 \times 10^{10} \Omega.$$

111. In the steady state situation, there is no current going to the capacitors, so the resistors all have the same current. By the loop rule,

$$20.0 \text{ V} = (5.00 \, \Omega)i + (10.0 \, \Omega)i + (15.0 \, \Omega)i$$

which yields $i = \frac{2}{3} \text{ A}$. Consequently, the voltage across the $R_1 = 5.00 \, \Omega$ resistor is $(5.00 \, \Omega)(2/3 \text{ A}) = 10/3 \text{ V}$, and is equal to the voltage V_1 across the $C_1 = 5.00 \, \mu\text{F}$ capacitor. Using Eq. 26-22, we find the stored energy on that capacitor:

$$U_1 = \frac{1}{2}C_1(V_1)^2 = \frac{1}{2}(5.00 \times 10^{-6})\left(\frac{10}{3}\right)^2 = 2.78 \times 10^{-5} \text{ J} .$$

Similarly, the voltage across the $R_2 = 10.0 \, \Omega$ resistor is $(10.0 \, \Omega)(2/3 \text{ A}) = 20/3 \text{ V}$ and is equal to the voltage V_2 across the $C_2 = 10.0 \, \mu\text{F}$ capacitor. Hence,

$$U_2 = \frac{1}{2}C_2(V_2)^2 = \frac{1}{2}(10 \times 10^{-6})\left(\frac{20}{3}\right)^2 = 2.22 \times 10^{-4} \text{ J} .$$

Therefore, the total capacitor energy is $U_1 + U_2 = 2.50 \times 10^{-4} \text{ J}$.

112. (a) Applying the junction rule twice and the loop rule three times, we obtain

$$\begin{aligned}i_1 - i_2 + i_4 + i_5 &= 0 \\i_3 + i_4 + i_5 &= 0, \\-16 \text{ V} + 4 \text{ V} + (7 \, \Omega)i_1 + (5 \, \Omega)i_2 &= 0, \\10 \text{ V} - 4 \text{ V} - (5 \, \Omega)i_2 + (8 \, \Omega)i_3 - (9 \, \Omega)i_4 &= 0, \\12 \text{ V} + (9 \, \Omega)i_4 - (4 \, \Omega)i_5 &= 0;\end{aligned}$$

(b) Examining the coefficients of the currents in the above relations, we find

$$[A] = \begin{bmatrix} 1 & -1 & 0 & 1 & 1 \\ 0 & 0 & 1 & 1 & 1 \\ 7 & 5 & 0 & 0 & 0 \\ 0 & -5 & 8 & -9 & 0 \\ 0 & 0 & 0 & 9 & -4 \end{bmatrix} \text{ ohms}, \quad [C] = \begin{bmatrix} 0 \\ 0 \\ 12 \\ -6 \\ -12 \end{bmatrix} \text{ volts};$$

(c) $i_1 = 306/427 \approx 0.717 \text{ A},$
 $i_2 = 426/305 \approx 1.40 \text{ A},$
 $i_3 = -1452/2135 \approx -0.680 \text{ A},$
 $i_4 = -1524/2135 \approx -0.714 \text{ A},$
 $i_5 = 2976/2135 \approx 1.39 \text{ A}$

113. (a) $V_9 = (9.00 \, \Omega)(|i_4|) = 6.43 \, \text{V};$

(b) $P_7 = (i_1)^2(7.00 \, \Omega) = 3.60 \, \text{W};$


(c) $(12.0 \, \text{V})(i_5) = 16.7 \, \text{W};$

(d) $-(4.00 \, \text{V})(i_2) = -5.60 \, \text{W};$

(e) a (see the true direction of the current labeled i_4)

114. (a) Next, we graph Eq. 27-4 (scaled by a factor of 100) for $\mathcal{E} = 2.0 \text{ V}$ and $r = 100 \Omega$ over the range $0 \leq R \leq 500 \Omega$. We multiplied the SI output of Eq. 27-4 by 100 so that this graph would not be vanishingly small with the other graph (see part (b)) when they are plotted together.

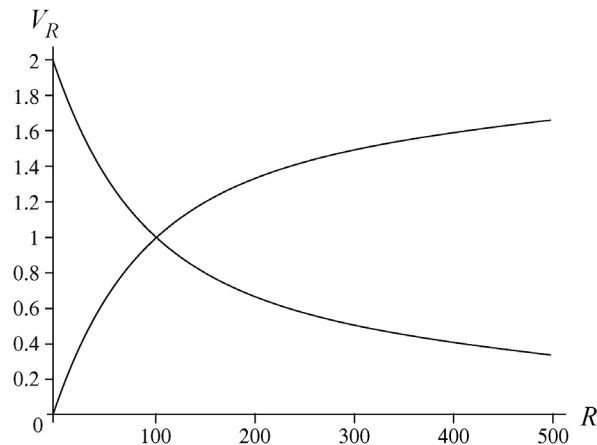(b) In the same graph, we show $V_R = iR$ over the same range. The graph of current i is the one that starts at 2 (which corresponds to 0.02 A in SI units) and the graph of voltage V_R is the one that starts at 0 (when $R = 0$). The value of V_R are in SI units (not scaled by any factor).



(c) In our final graph, we show the dependence of power $P = iV_R$ (dissipated in resistor R) as a function of R . The units of the vertical axis are Watts. We note that it is maximum when $R = r$.

